

# CSE211 Digital Design

Akdeniz University

Week10: Combinational Logic Part 1

1

Assoc.Prof.Dr. Taner Danişman

tdanisman@akdeniz.edu.tr

# Course program

2

Week 01	2-Oct-23	Introduction
Week 02	9-Oct-23	Digital Systems and Binary Numbers I
Week 03	16-Oct-23	Digital Systems and Binary Numbers II
Week 04	23-Oct-23	Boolean Algebra and Logic Gates I
Week 05	30-Oct-23	Boolean Algebra and Logic Gates II
Week 06	6-Nov-23	Gate Level Minimization
Week 07	13-Nov-23	Karnaugh Maps
Week 08	20-Nov-23	Midterm
Week 09	27-Nov-23	Karnaugh Maps
Week 10	4-Dec-23	Combinational Logic
Week 11	11-Dec-23	Combinational Logic
Week 12	18-Dec-23	Timing, delays and hazards
Week 13	25-Dec-23	Synchronous Sequential Logic
Week 14	1-Jan-24	Synchronous Sequential Logic

# Terms to know

3

- ASIC
- MSI
- VLSI

AUGEND	→	6
ADDEND	→	3
<hr/>		
SUM	→	9

DIVIDEND	→	18
DIVISOR	→	3
<hr/>		
QUOTIENT	→	6

MINUEND	→	9
SUBTRAHEND	→	3
<hr/>		
DIFFERENCE	→	6

MULTIPLICAND	→	6
MULTIPLIER	→	3
<hr/>		
PRODUCT	→	18

# Classifications

4

## ➤ **Combinational Logic**


- **No memory** unit
- Expressed by Boolean functions
- Outputs depends on only the **present** inputs

## ➤ **Sequential Logic**

- Storage elements + logic gates
- The content of the storage elements define the state of the circuit
- Outputs are functions of both input and current state
- State is a function of previous inputs
- Outputs not only depend the present inputs but also the past inputs
- Time sequence of inputs and internal states

# Combinational Circuit

5

 

- $n$  input bits  $\rightarrow 2^n$  possible binary input combinations
- $m$  output variable produced
  - For each possible input combination, there is one possible output value
    - truth table
    - Boolean functions (with  $n$  input variables)
- **Examples: adders, subtractors, comparators, decoders, encoders, and multiplexers.**

# So Far...

6

- **Chapter #1** binary numbers and binary codes that represent discrete quantities of information.
- **Chapter #2** Boolean algebra as a way to express logic functions algebraically
- **Chapter #3** How to simplify Boolean functions to achieve economical (simpler) gate implementations.
- **Chapter #4** to use the knowledge acquired in previous chapters to formulate systematic analysis and design procedures for combinational circuits
  - Analyze the behavior of a given logic circuit
  - synthesize a circuit that will have a given behavior
  - Write hardware description language (HDL) models

# Analysis & Design of Combinational Logic

7

- **Analysis: to find out the function that a given circuit implements**
  - We are given a logic circuit and we are expected to find out
    1. Boolean function(s)
    2. Truth table
    3. A possible explanation of the circuit operation (i.e. what it does)
- Firstly, make sure that the given circuit is, **indeed, combinational.**



# Analysis of Combinational Logic


8

- Verifying the circuit is combinational
  - Diagram has **no memory elements**
  - **No feedback paths** (connections)
    - A feedback path is a connection from the output of one gate to the input of a second gate whose output forms part of the input to the first gate
- Secondly, obtain a Boolean function for each output or the truth table
- Lastly, interpret the operation of the circuit from the derived Boolean functions or truth table
  - What is it the circuit doing?
  - Addition, subtraction, multiplication, etc.
- The analysis can be performed by using a computer program



# Example: Obtaining Boolean Function

9

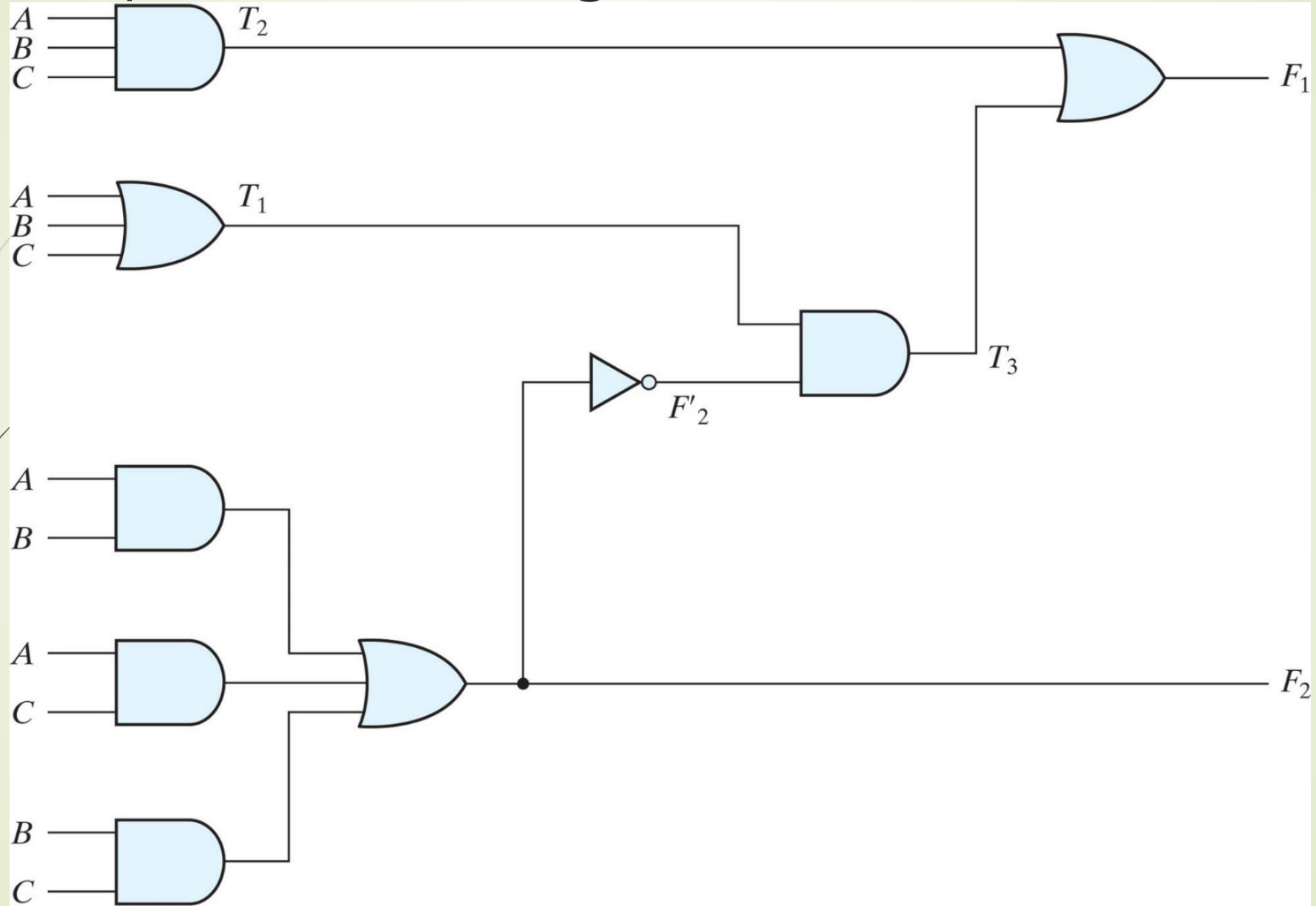

# Example: Obtaining Boolean Function

10

## Boolean expressions for named wires

■  $T_1 = a + b + c$

■  $T_2 = abc$

■  $F_2 = ab + ac + bc$

■  $T_3 = F'_2 T_1 = (ab + ac + bc)' (a + b + c)$


■  $F_1 = T_2 + T_3$

$$= abc + (ab + ac + bc)' (a + b + c)$$

$$= abc + ((a' + b')(a' + c')(b' + c')) (a + b + c)$$

$$= abc + ((a' + a'c' + a'b' + b'c')(b' + c')) (a + b + c)$$
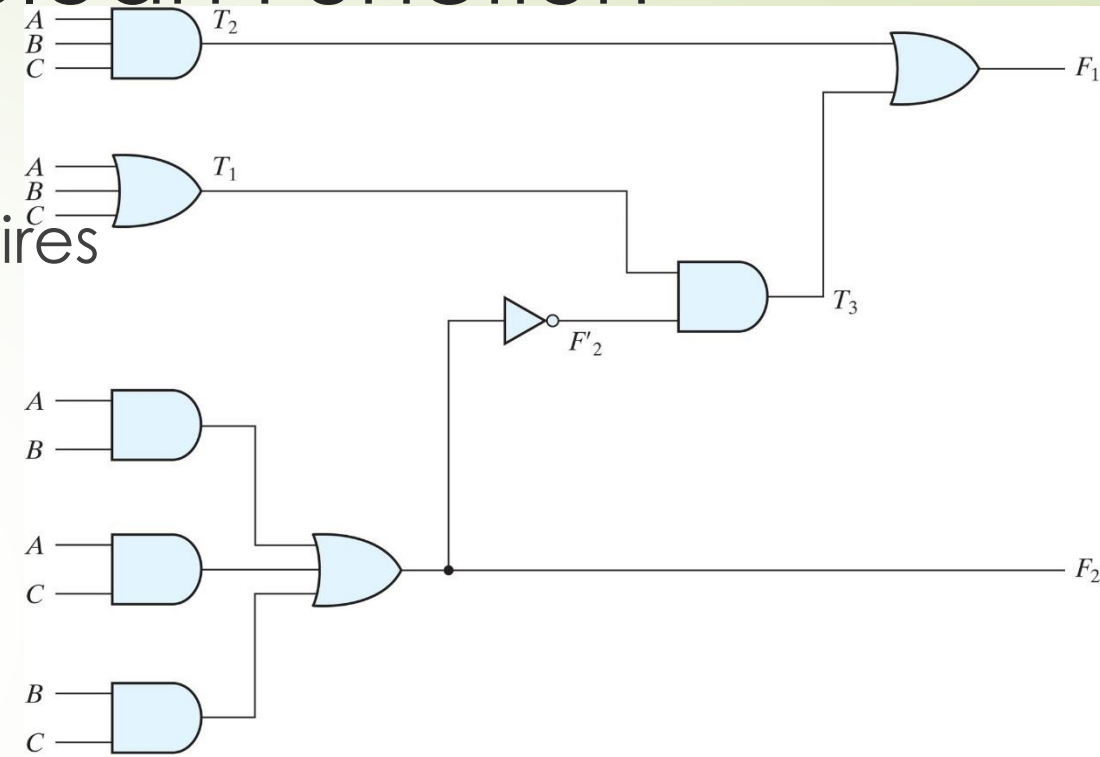
$$= abc + (a'b' + a'c' + a'b'c' + b'c') (a + b + c)$$



Copyright ©2013 Pearson Education, publishing as Prentice Hall

# Example: Obtaining Boolean Function

11

**Table 4.1**

*Truth Table for the Logic Diagram of Fig. 4.2*

<b>A</b>	<b>B</b>	<b>C</b>	<b>F<sub>2</sub></b>	<b>F'<sub>2</sub></b>	<b>T<sub>1</sub></b>	<b>T<sub>2</sub></b>	<b>T<sub>3</sub></b>	<b>F<sub>1</sub></b>
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

Copyright ©2012 Pearson Education, publishing as Prentice Hall

➡ This is what we call **full-adder** (FA)

# Design of Combinational Logic

12

- We start with the verbal specification about what the resulting circuit will do for us (i.e. which function it will implement)
  - Specifications are often verbal, and **very likely incomplete** and **ambiguous (if not faulty)**
  - **Wrong interpretations** can result in **incorrect circuit**
- We are expected to find
  1. **Boolean function(s)** (or **truth table**) to realize the desired functionality
  2. **Logic circuit** implementing the Boolean function(s) (or the truth table)

# Design Constraints

13

- From the truth table, we can obtain a **variety of simplified expressions**
- Question: which one to choose?
- The design constraints may help in the selection process
- **Constraints:**
  - number of gates
  - propagation time of the signal all the way from the inputs to the outputs
  - number of inputs to a gate
  - number of interconnections
  - power consumption
  - driving capability of each gate

# Code Conversion Example

14

- To convert from binary code A to binary code B
- A combinational circuit performs this transformation by means of logic gates

**Table 4.2**

*Truth Table for Code Conversion Example*

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0



# Code Conversion Example

- Find the boolean functions for w, x, y, and z

AB \ CD		C			
		00	01	11	10
A	00	$m_0$ 1	$m_1$	$m_3$	$m_2$ 1
	01	$m_4$ 1	$m_5$	$m_7$	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$	$m_{11}$ X	$m_{10}$ X

$z = D'$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$ 1	$m_1$	$m_3$ 1	$m_2$
	01	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$	$m_{11}$ X	$m_{10}$ X

$y = CD + C'D'$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$	$m_1$ 1	$m_3$ 1	$m_2$ 1
	01	$m_4$ 1	$m_5$	$m_7$	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$	$m_9$ 1	$m_{11}$ X	$m_{10}$ X

$x = B'C + B'D + BC'D'$


AB \ CD		C			
		00	01	11	10
A	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$ 1	$m_7$ 1	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$ 1	$m_{11}$ X	$m_{10}$ X

$w = A + BC + BD$



# Logic diagram for BCD-to-excess-3 code converter

16

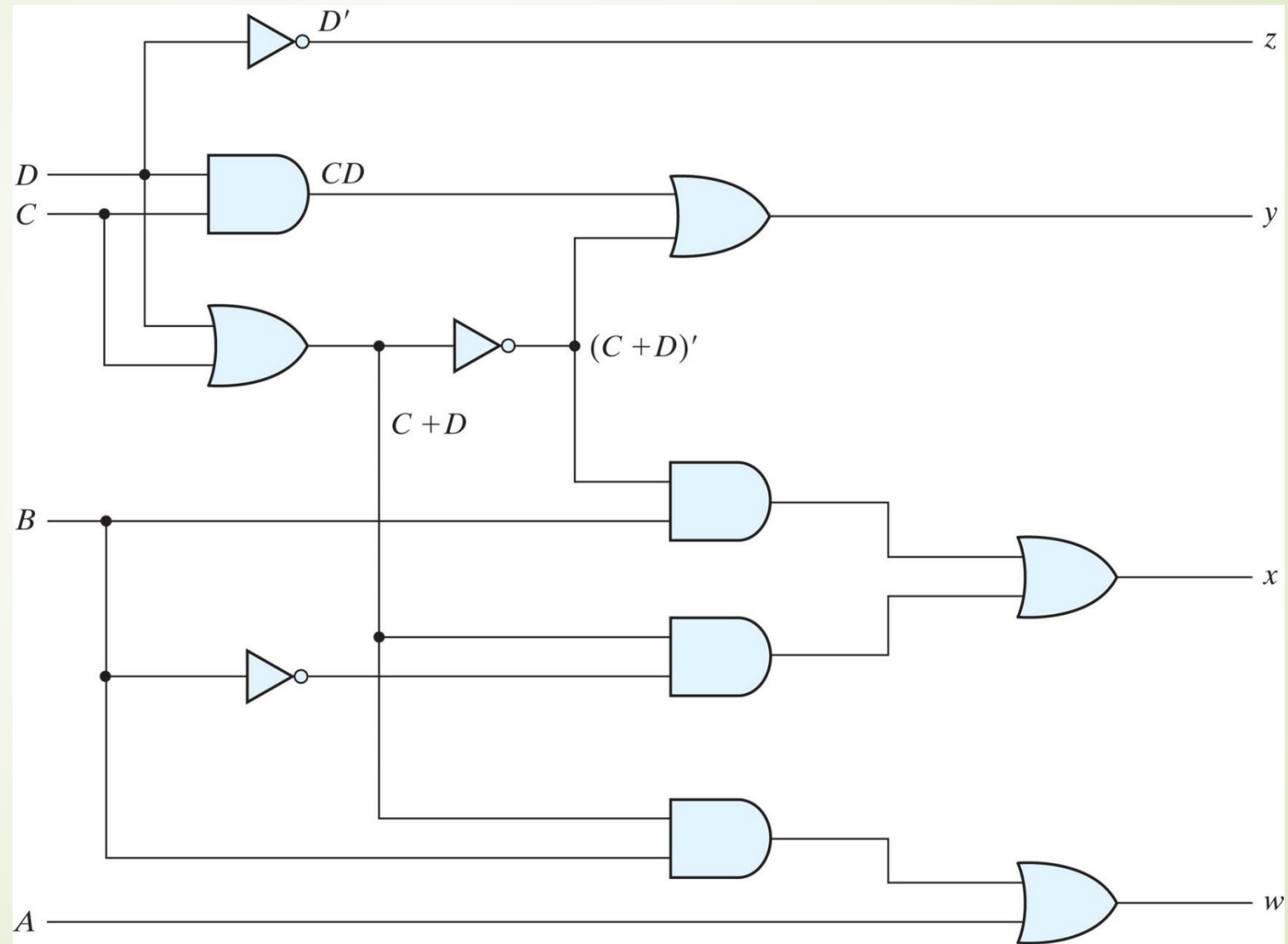

# Binary Adder and Subtractor

17

- **(Arithmetic) Addition** of two binary digits
  - $0 + 0 = 0$ ,  $0 + 1 = 1$ ,  $1 + 0 = 1$ , and  $1 + 1 = 10$
  - The result has two components
    - the sum (S)
    - the carry (C)
- A combinational circuit that performs the addition of two bits is called a **half adder**
- One that performs the addition of three bits (two significant bits and a previous carry) is a **full adder**
- **Two half adders** can be employed to implement a **full adder**.

# Half Adder

18

- The result has two components
  - the sum (S)
  - the carry (C)

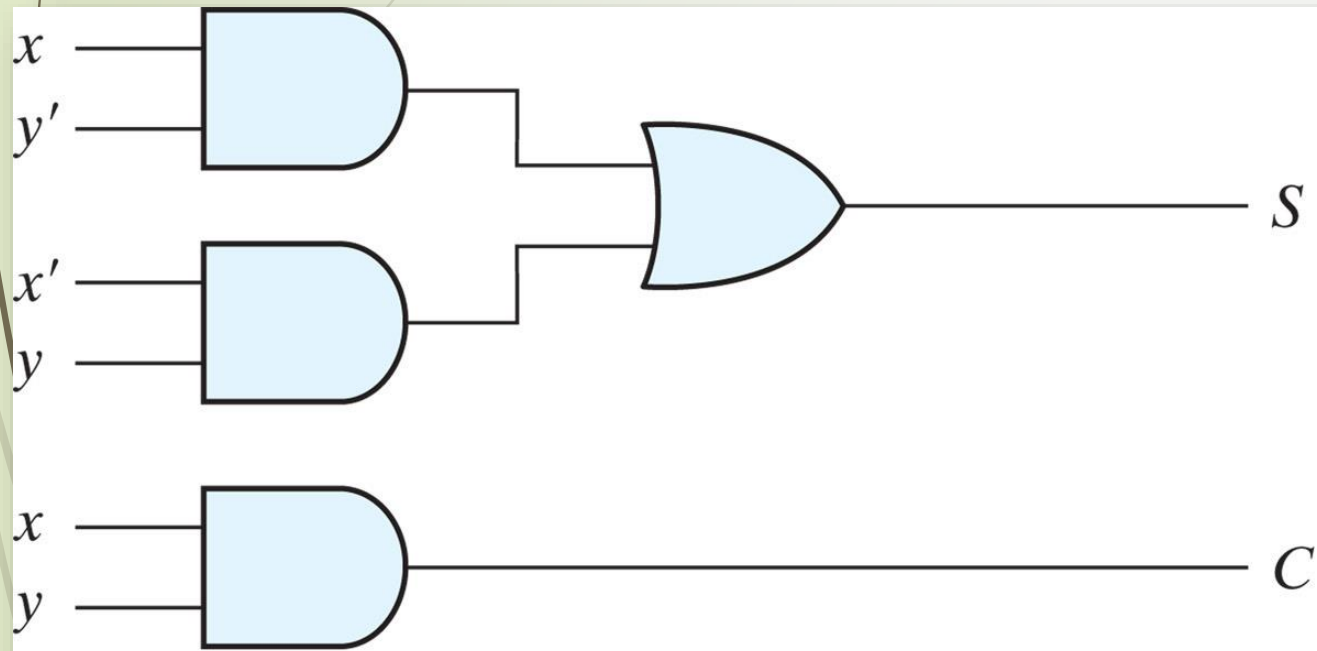


**Table 4.3**  
*Half Adder*


<b><i>x</i></b>	<b><i>y</i></b>	<b><i>c</i></b>	<b><i>s</i></b>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
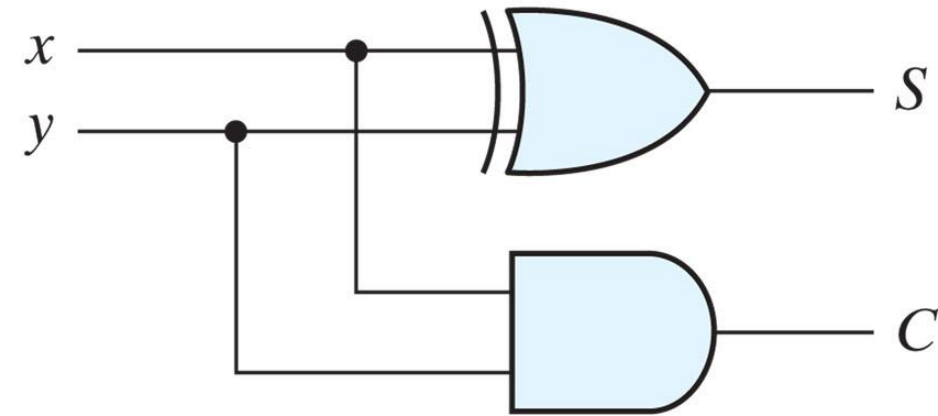
# Half Adder (Cont.)

19



$$(a) \begin{aligned} S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$(b) \begin{aligned} S &= x \oplus y \\ C &= xy \end{aligned}$$

# Full Adder

20

- A circuit that performs the arithmetic sum of **three bits**
  - Three inputs
  - the range of output is **[0, 3]**
  - Two binary outputs

**Table 4.4**  
*Full Adder*

<b>x</b>	<b>y</b>	<b>z</b>	<b>C</b>	<b>S</b>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# K-Map for Full Adder

21

		$y$			
		$yz$	00	01	11
$x$	0	$m_0$	$m_1$ 1	$m_3$	$m_2$ 1
	1	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$
		$z$			

(a)  $S = x'y'z + x'yz' + xy'z' + xyz$


		$y$			
		$yz$	00	01	11
$x$	0	$m_0$	$m_1$	$m_3$ 1	$m_2$
	1	$m_4$	$m_5$ 1	$m_7$ 1	$m_6$ 1

$z$


(b)  $C = xy + xz + yz$

# Implementation of full adder in sum-of-products form

22

 


(a)  $S = x'y'z + x'yz' + xy'z' + xyz$

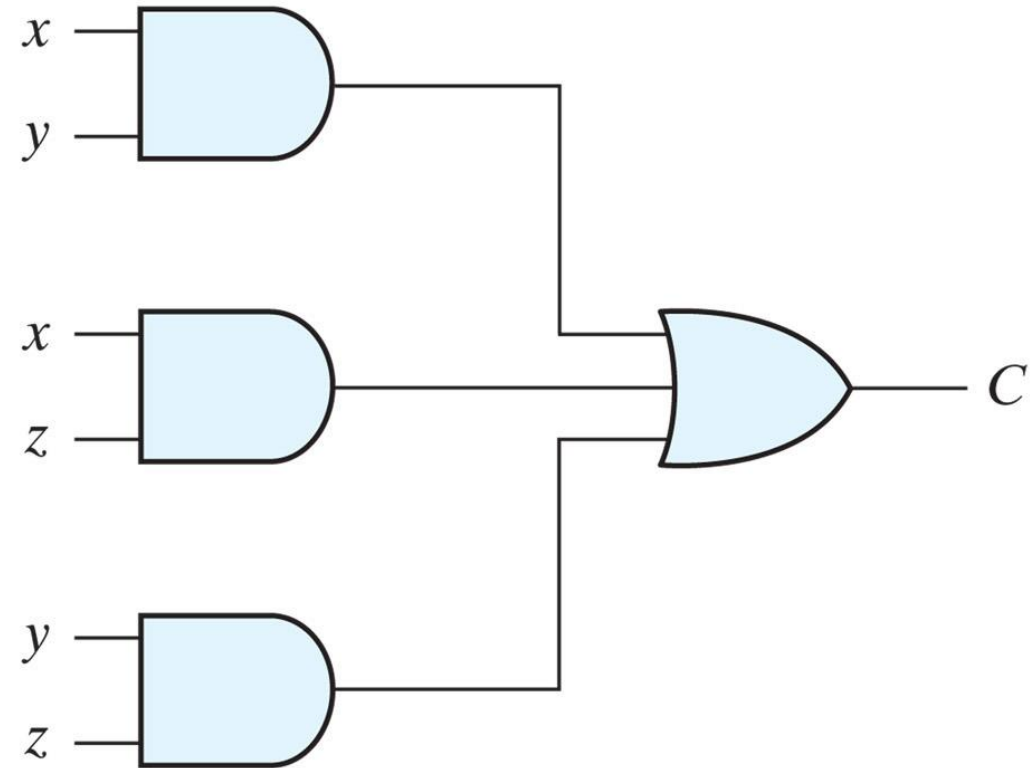

(b)  $C = xy + xz + yz$


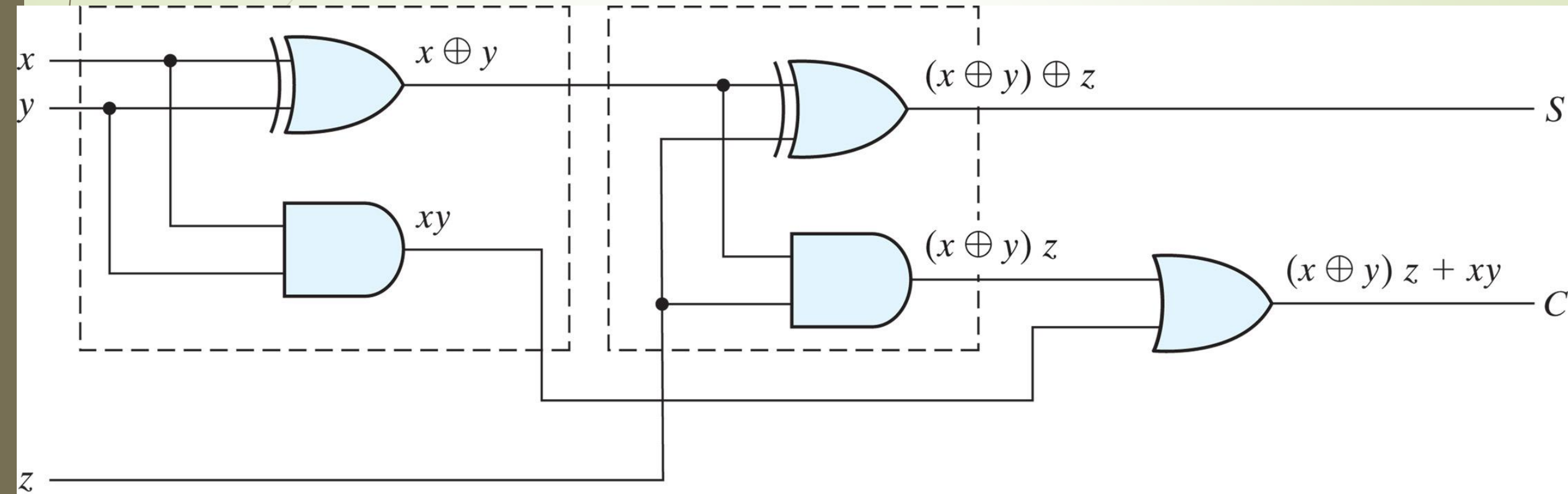
# Implementation of full adder with two half adders and an OR gate



# Binary Adders

24

- The design methodology we used to build carry-ripple adder is what is referred as **hierarchical design.**
- To add two 4-bit numbers, in classical design, we have:
  - 9 inputs including  $C_0$ .
  - 5 outputs
  - Truth tables with  $2^9 = 512$  entries
  - We have to optimize five Boolean functions with 9 variables each.
- In Hierarchical design
  - we divide our design into smaller functional blocks
  - connect functional units to produce the big functionality

# Binary adders


25

- A digital circuit that produces the arithmetic sum of two binary numbers

- $A = (a_{n-1}, a_{n-2}, \dots, a_1, a_0)$

- $B = (b_{n-1}, b_{n-2}, \dots, b_1, b_0)$

- A simple case: 4-bit binary adder

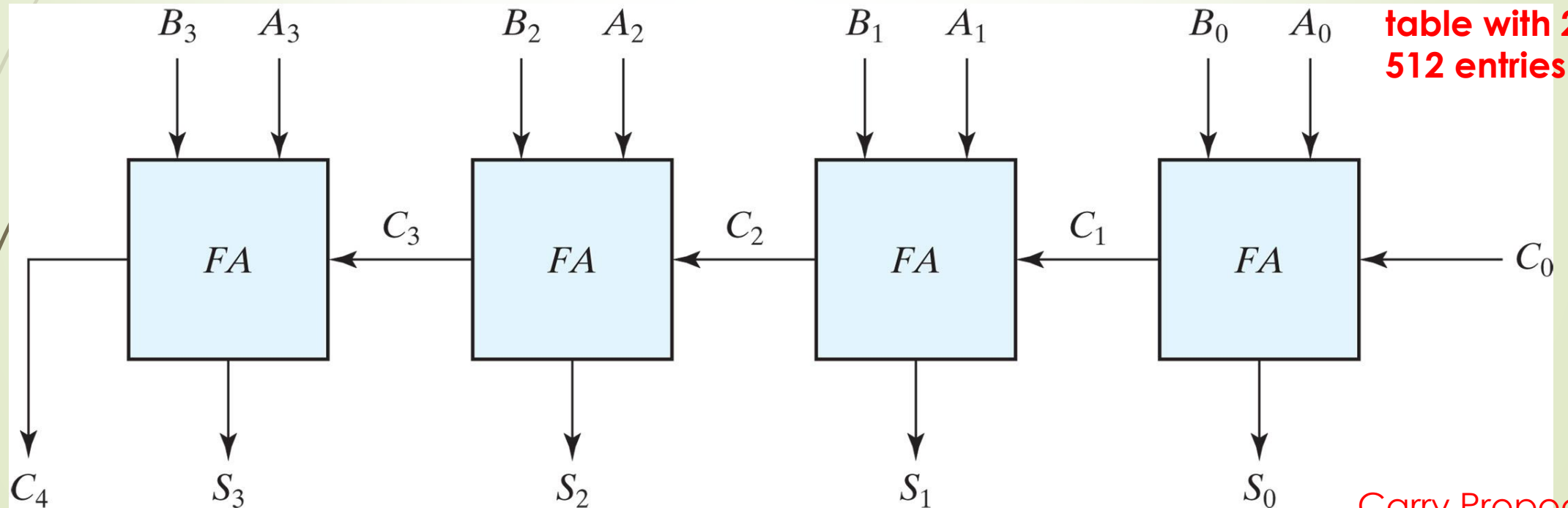

**Design of this circuit by the classical method would require a truth table with  $2^9 = 512$  entries**

**Carry Propagation!**

# Binary Adders

26

- Consider the two binary numbers **A = 1011**, and **B = 0011**. Their sum **S = 1110** is formed with the four-bit adder as follows

Subscript <i>i</i> :	3	2	1	0	
Input carry	0	1	1	0	$C_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$

# Carry Propagation


27

- The addition of two binary numbers in parallel implies that all the bits of the **augend** and **addend** are available for computation at the same time
- Sum output will be in its **steady-state final value** only after the input carry to that stage has been propagated
- The **outputs will not be correct** unless the signals are given enough time to **propagate** through the gates connected from the inputs to the outputs
- Solution is to use **carry lookahead logic**
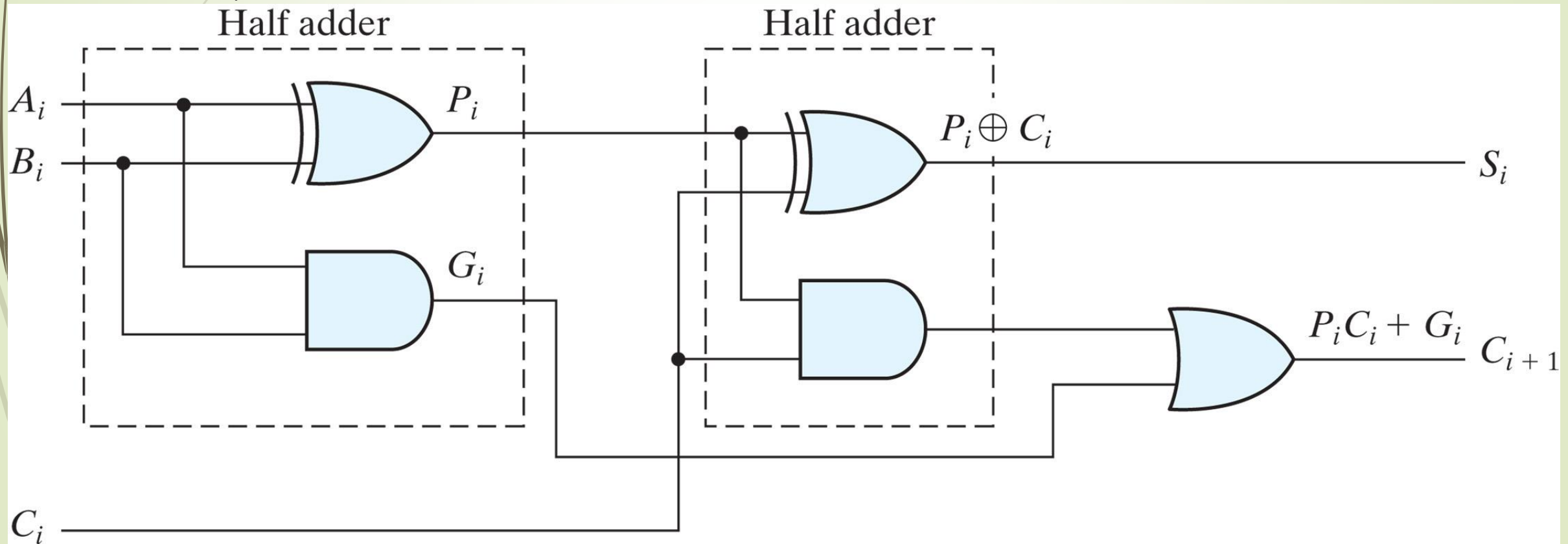
# Carry Propagation

28

- $G_i$  is called a **carry generate**
- $P_i$  is called a **carry propagate**



# Carry Lookahead Generator

29

- $C_3$  does not have to wait for  $C_2$  and  $C_1$  to propagate
- This **gain** in speed of operation is achieved at the expense of additional **complexity** (hardware).

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

$$C_0 = \text{input carry}$$


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$


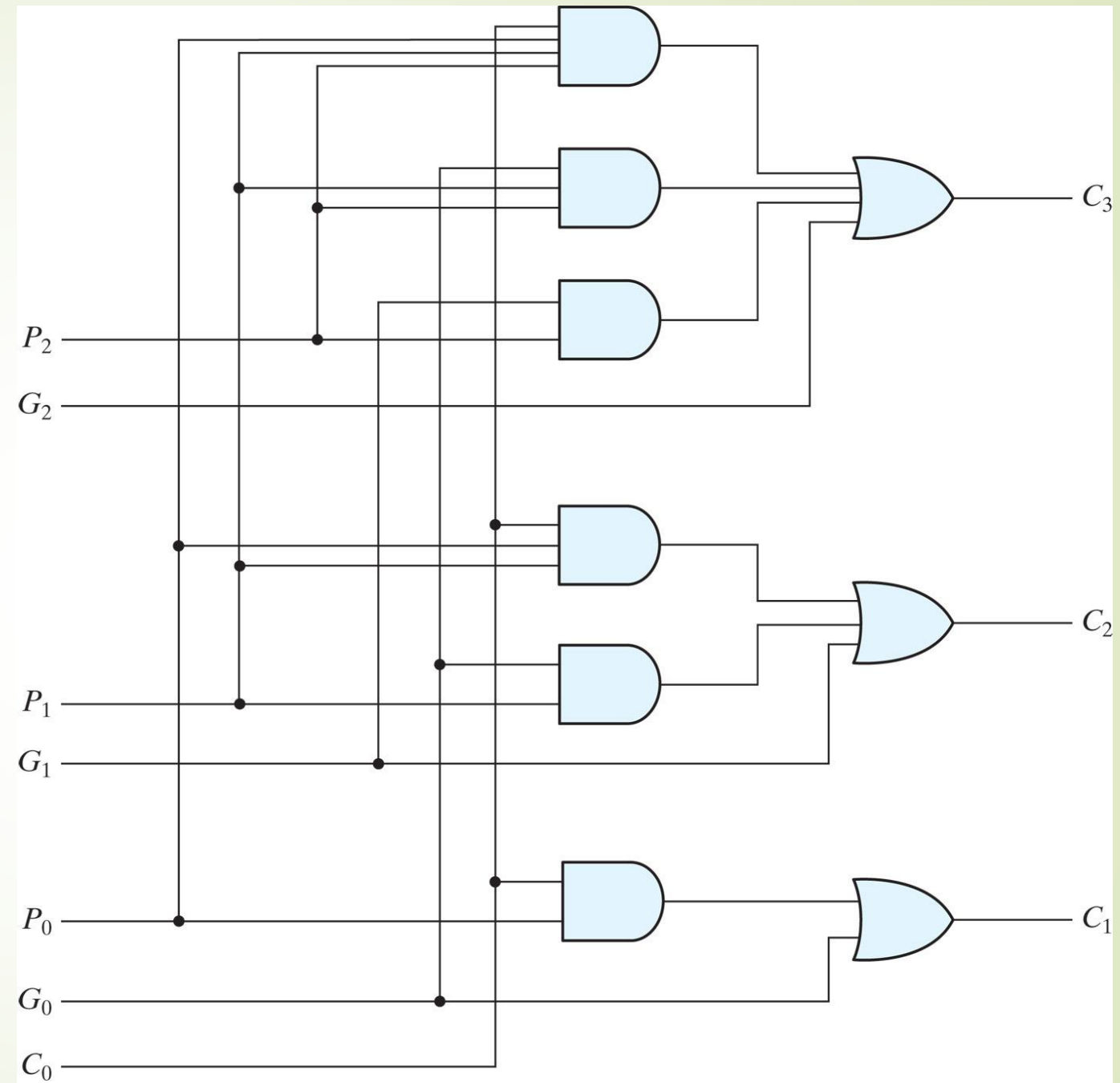
# Logic diagram of carry lookahead generator



# Four-bit adder with carry look ahead

