



## Lab06 – Synchronous Sequential Logic – 20.12.2024


	Student No	Student Full Name	Group No
1	Yahya Efe Kuruçay	20220808005	4
2	Burak Yalçın	20220808069	
3	Alp Bora Emrize	20220808014	
4			

Lab Study 1 - Understanding the 7474 D-Type Flip-Flop

**Task:** Observe and verify the basic operation of the 7474 D Flip-Flop.

**Circuit Setup:**

- Connect Vcc to 5V and GND to ground.
- Connect D, CLR and PR to switches:
  - D: Data input.
  - CLK: Clock input.
  - CLR: Active-low reset.
  - PR: Active-low set.
- Attach LEDs to Q and Q' outputs to observe the flip-flop's state.

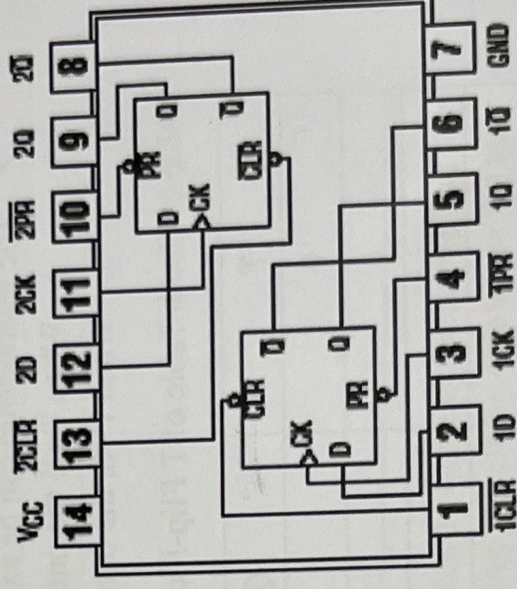**Input Test Cases:**

- Apply different combinations of D, CLR, and PR.


Table 1 - Truth Table of D Flip-Flop

CLR	PR	CLK	D	Q	Q'
0	1	X	X		
1	0	X	X		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		



## Lab Study 2 - Using the D Flip-Flop as a T Flip-Flop

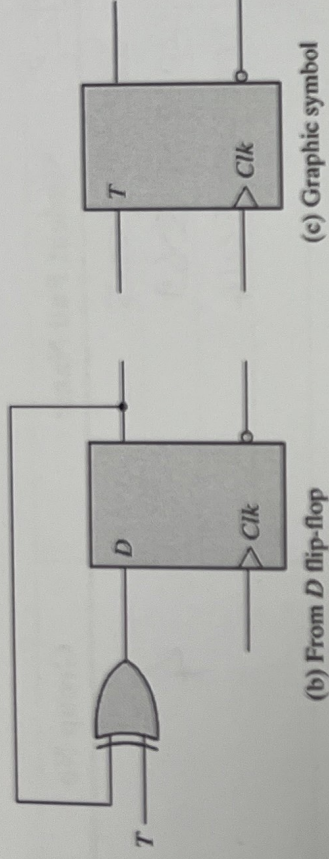**Task:** Convert the D Flip-Flop into a T Flip-Flop using an XOR gate. The circuit diagram is given below. Build the circuit and observe the behavior of T Flip-Flop. Then fill the truth table.




### Concept:

- A T Flip-Flop toggles its output on each clock pulse if  $T=1$ .
- The relationship can be expressed as  $D=T \oplus Q$ 
  - When  $T=1$ , the output toggles.
  - When  $T=0$ , the output remains unchanged.

Table 2 - Truth Table of T Flip-Flop

$T$	$Q(t)$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0


## 74LS86 Pinout

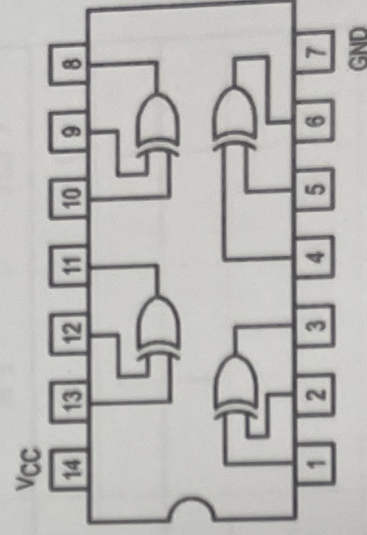



### Lab Study 3 - Designing a Binary Counter Using T Flip-Flops

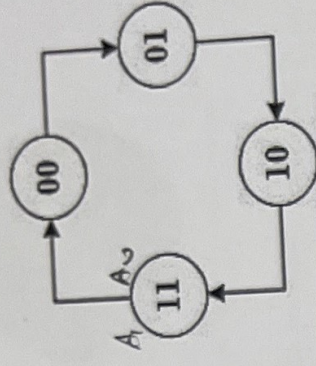**Task:** Build a 2-bit binary counter using T Flip-Flops. The state diagram of the counter is given.



Based on the state machine diagram

1. Fill out the truth table below

Present State		Next State		Flip-Flop Inputs	
$A_1$	$A_0$	$A_1$	$A_0$	$T_{A_1}$	$T_{A_0}$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

2. Draw the K-Maps and find the functions of  $T_{A_0}$  and  $T_{A_1}$ .

$T_{A_1}$	$T_{A_0}$

3. Complete the circuit diagram of the 2-bit binary counter. Then build the circuit and observe the counter's behavior. Show the numbers using 7-segment display on the test set.

