



**Lab04 – Combinational Logic – 25.11.2024**

	Student No	Student Full Name	Group No
1			
2			
3			
4			

**Lab Study 1 – 3x8 Decoder**

Design and implement a 3-to-8 decoder circuit using the 74138 IC and analyze its functionality. Then, fill in the truth table below.

INPUTS				OUTPUTS (LEDs)							
A	B	C	E	D0	D1	D2	D3	D4	D5	D6	D7
X	X	X	0								
0	0	0	1								
0	0	1	1								
0	1	0	1								
0	1	1	1								
1	0	0	1								
1	0	1	1								
1	1	0	1								
1	1	1	1								

**74LS138 (3x8 Decoder)**

