



Lab05 – Combinational Logic – 16.12.2024

	Student No	Student Full Name	Group No
1			
2			
3			
4			

Lab Study 1 – 4-bit Adder

Design and test a 4-bit binary adder circuit using the 74LS83 IC. Understand functionality of the binary addition and carry propagation through a practical implementation. Fill the truth table for 4 different 4-bit binary summing operation. (C0 should be connected to ground)

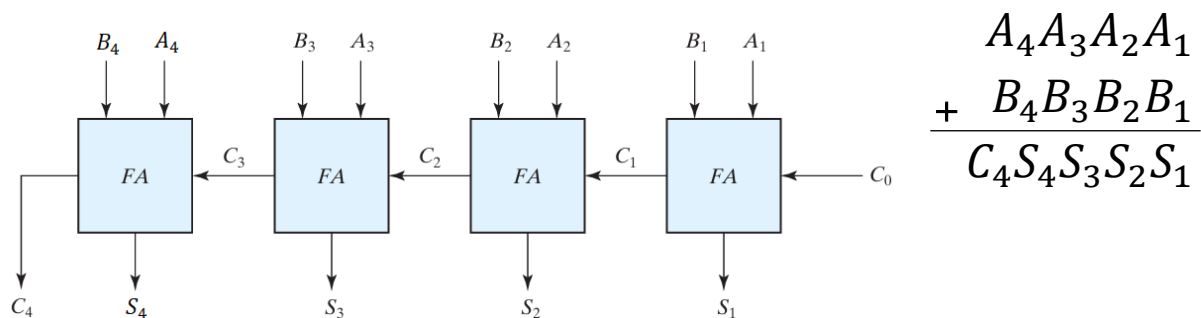


Figure 1: 4-Bit Adder

4-Bit Adder Truth Table (Fill the table for only 4 different 4-bit adding operation)

C_0	A_4	A_3	A_2	A_1	B_4	B_3	B_2	B_1	C_4	S_4	S_3	S_2	S_1
0													
0													
0													
0													

Lab Study 2 – 8x1 Multiplexer

Design 8x1 multiplexer circuit by using 74LS151 IC for data selection task.

Steps:

1. Circuit Setup

- Connect 8 input switches to D0–D7, representing data inputs.
- Connect **select lines** (S0, S1, S2) to three separate switches.
- Attach LEDs to Y and Y' (W) to observe the selected output and its complement.

2. Input Test Cases

- Apply different binary combinations to the select lines (S0, S1, S2).
- Verify that the output corresponds to the selected input line.
- Fill out the truth table below.

Strobe	S_0	S_1	S_2	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	Y	W
	0	0	0										
	0	0	1										
	0	1	0										
	0	1	1										
	1	0	0										
	1	0	1										
	1	1	0										
	1	1	1										

IC Pinouts

