

Asynchronous Counters



Lecture Overview

- Classifications of Counters
- Definitions
- Asynchronous Counter...
 - J – K Flip Flops
 - D Flip Flops
 - Up Counters
 - Down Counters
 - Truncated Counters



Classifications of Counters

Asynchronous Counters

- Only the first flip-flop is clocked by an external clock. All subsequent flip-flops are clocked by the output of the preceding flip-flop.
- Asynchronous counters are slower than synchronous counters because of the delay in the transmission of the pulses from flip-flop to flip-flop.
- Asynchronous counters are also called *ripple-counters* because of the way the clock pulse ripples it way through the flip-flops.



Classifications of Counters

Synchronous Counters

- All flip-flops are clocked simultaneously by an external clock.
- Synchronous counters are faster than asynchronous counters because of the simultaneous clocking.
- Synchronous counters are an example of *state machine* design because they have a set of states and a set of transition rules for moving between those states after each clocked event.





States / Modulus / Flip-Flops

- The number of flip-flops determines the count limit or number of states.



$$(\text{STATES} = 2^{\text{\# of flip flops}})$$

- The number of states used is called the *MODULUS*.
- For example, a Modulus-12 counter would count from 0 (0000) to 11 (1011) and requires four flip-flops (16 states - 12 used).



1 Bit Asynch-Counter / Modulus 2

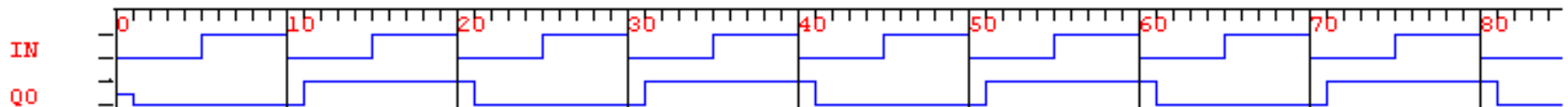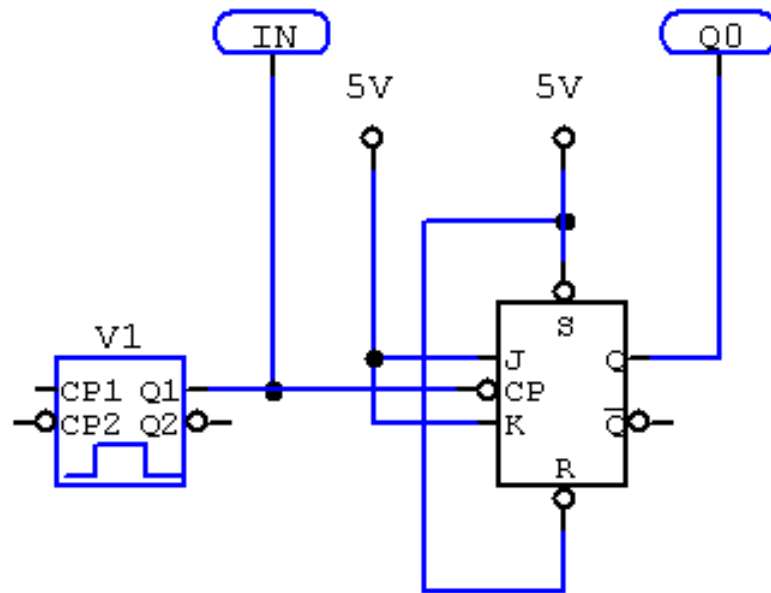



2 Bit Asynch-Counter / Modulus 4

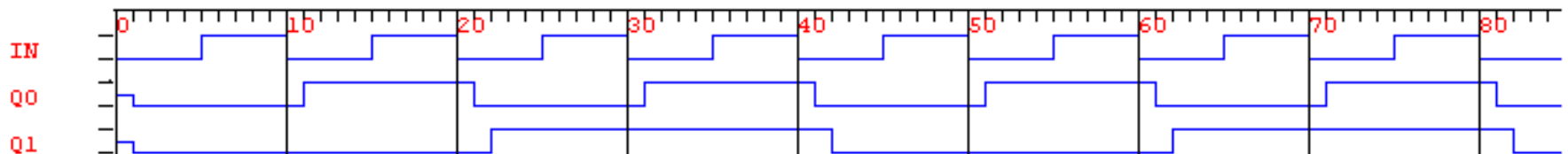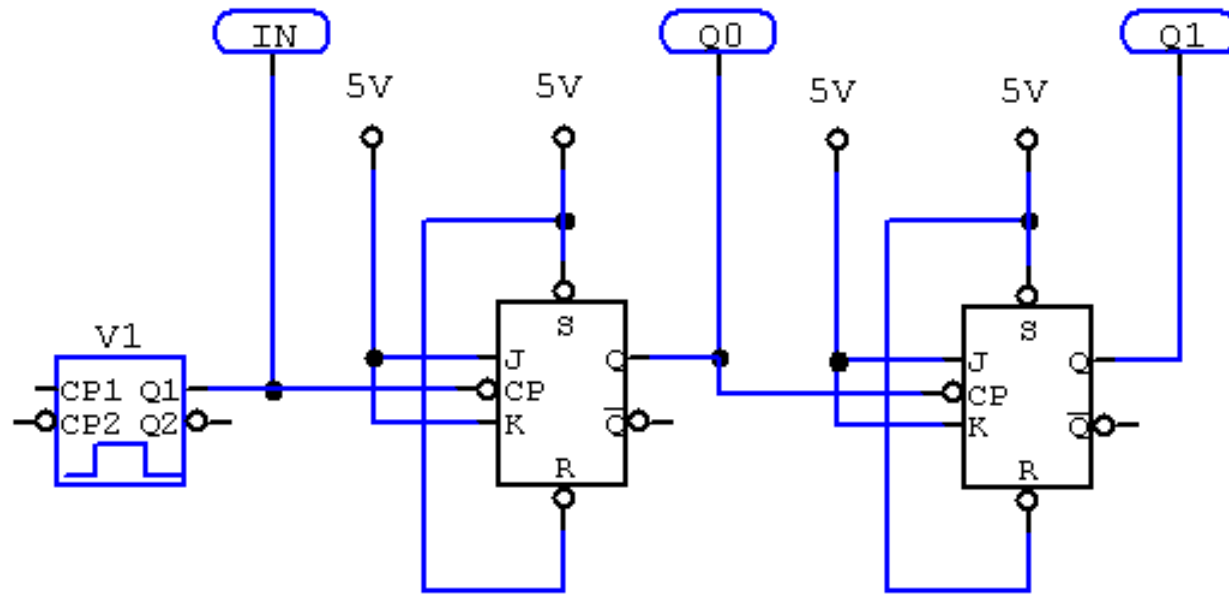

3 Bit Asynch-Counter / Modulus 8

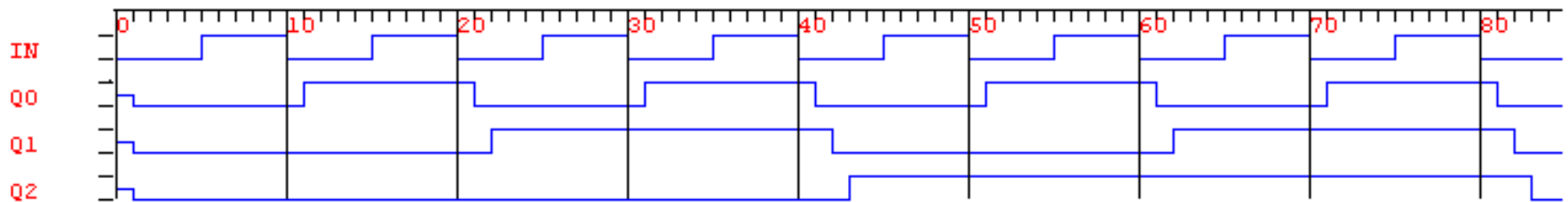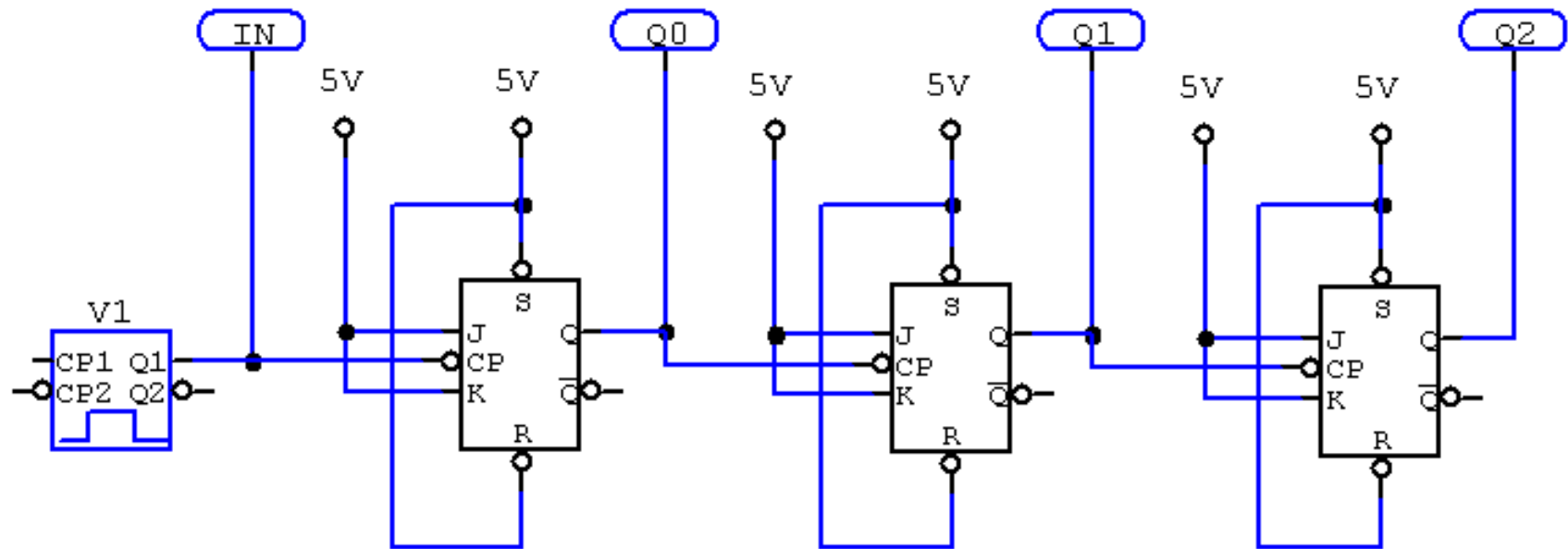

D Flip-Flop... Nothing Special About J-K

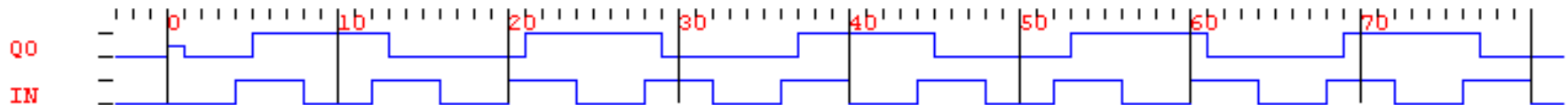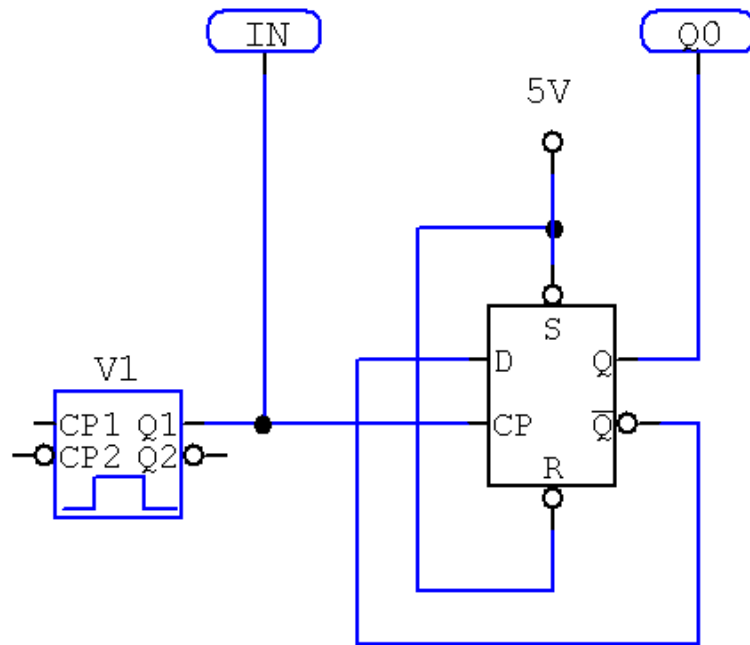





Six Examples

1. Modulus 4 Up Counter with Negative Edge Triggered Flip-Flops
2. Modulus 4 Down Counter with Negative Edge Triggered Flip-Flops
3. Modulus 4 Up Counter with Positive Edge Triggered Flip-Flops
4. Modulus 4 Down Counter with Positive Edge Triggered Flip-Flops
5. Truncated Counter
6. Counter Design


Up Counter w/ Negative Edge Flip-Flops

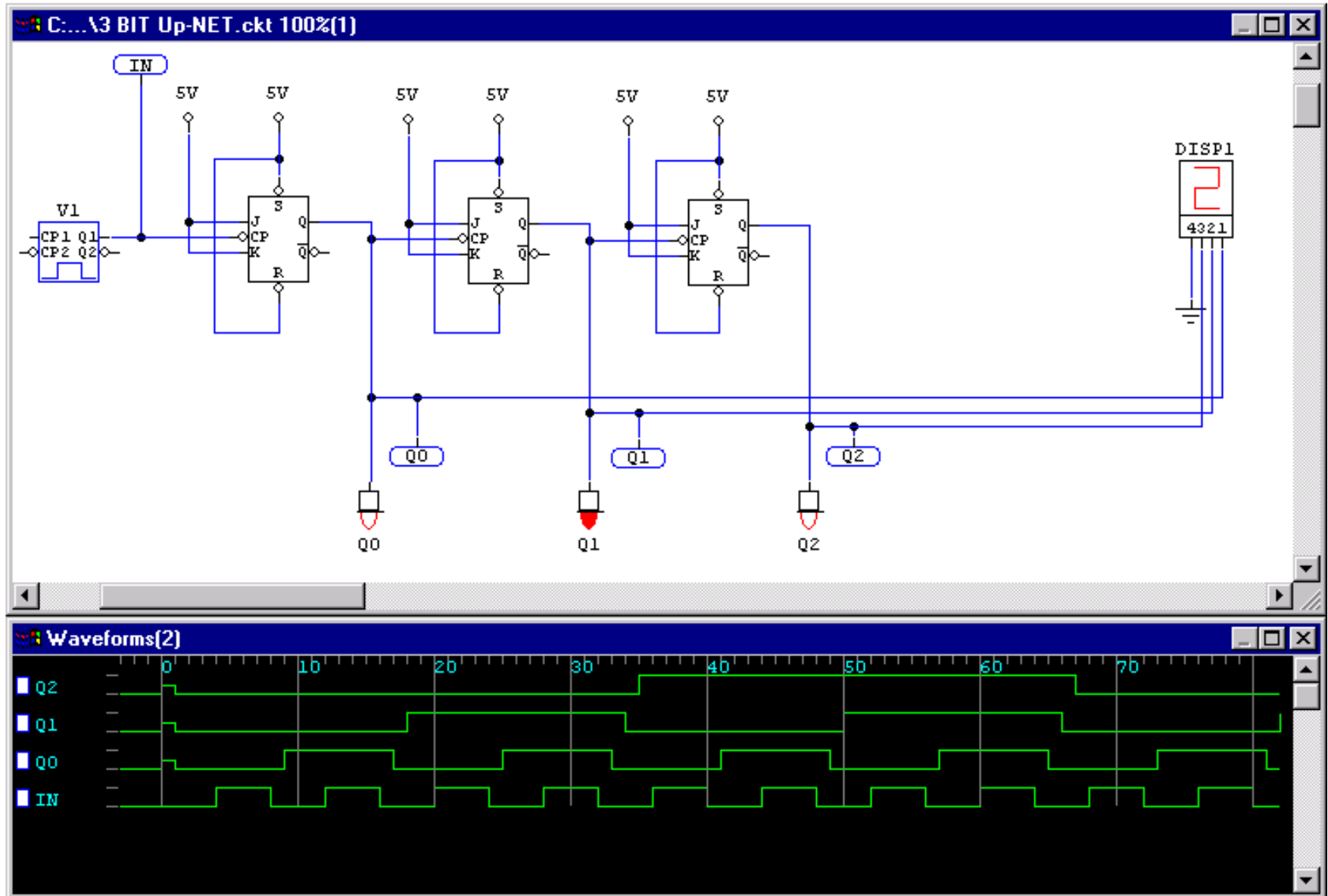


Down Counter w/ Negative Edge Flip-Flops

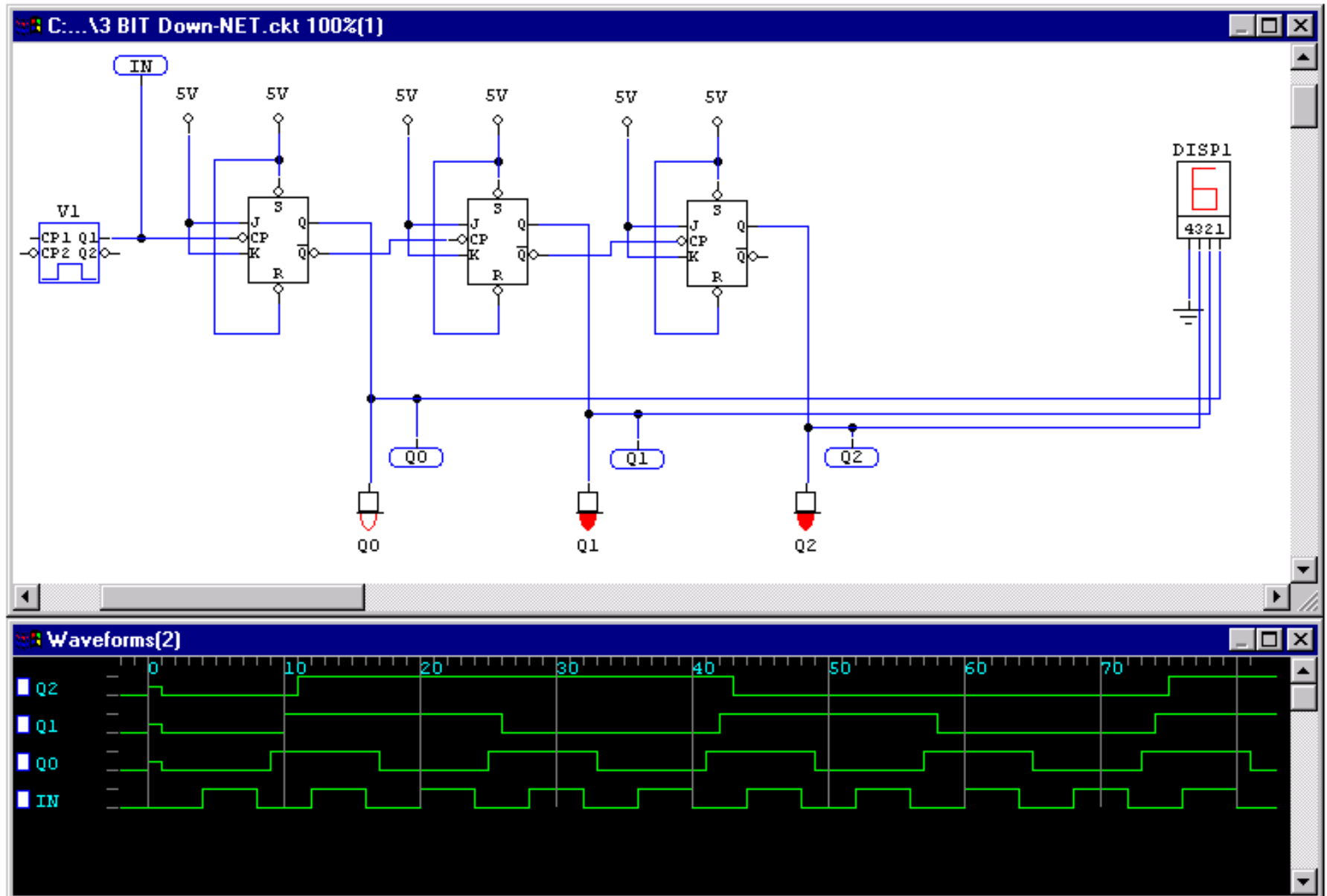


Up Counter w/ Positive Edge Flip-Flops

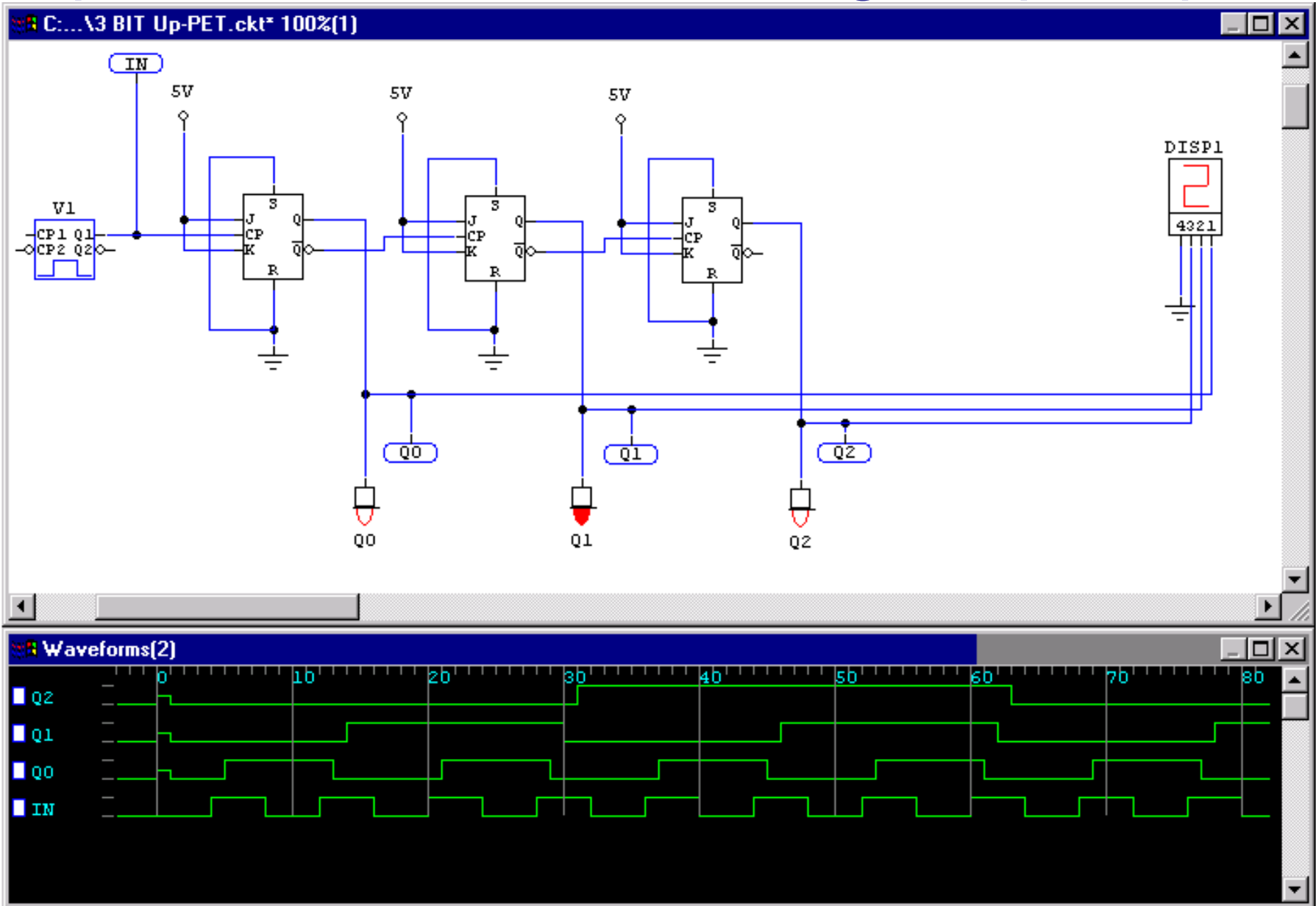

Down Counter w/ Positive Edge Flip-Flops

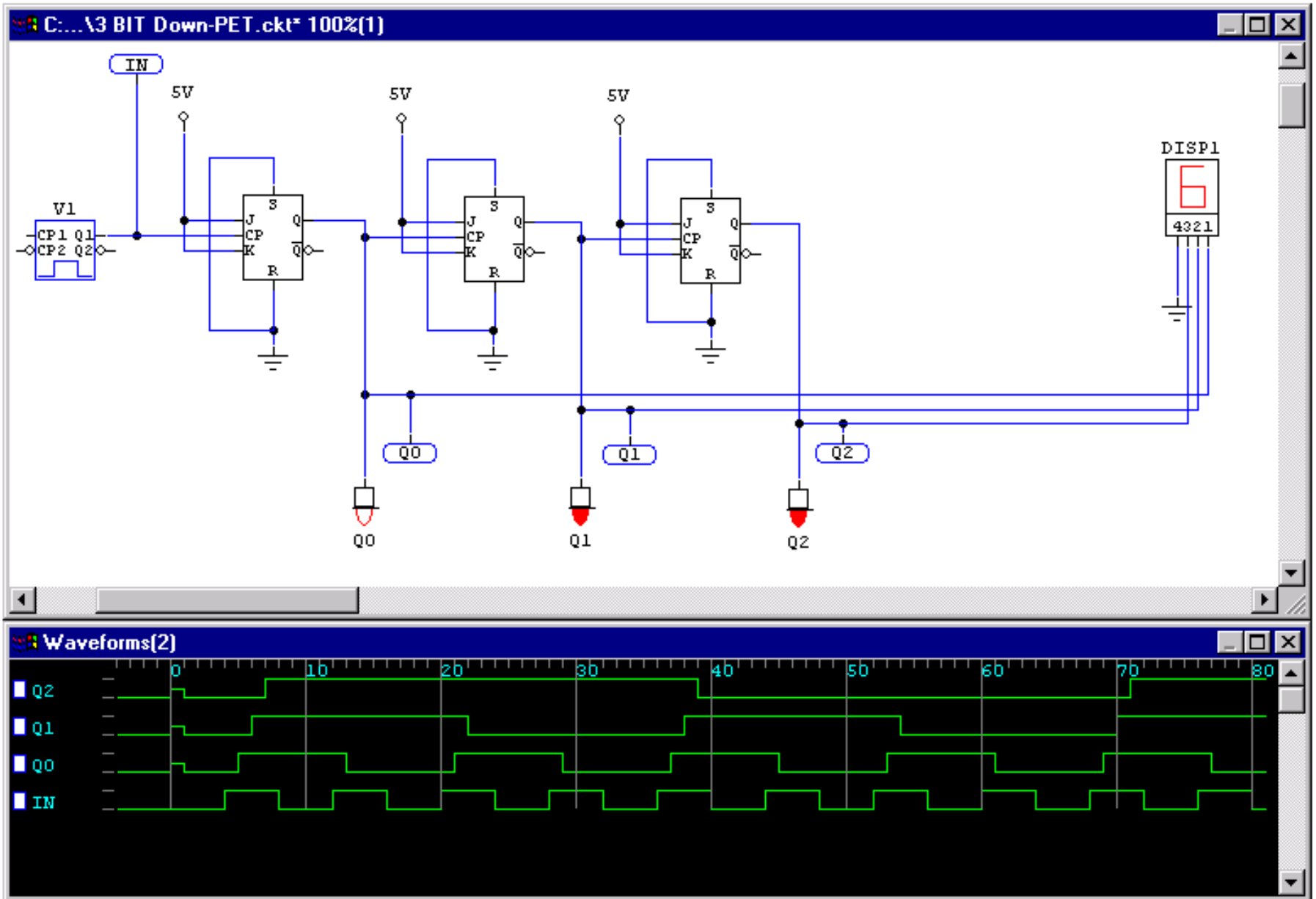

Truncating the Count... Modulus 6

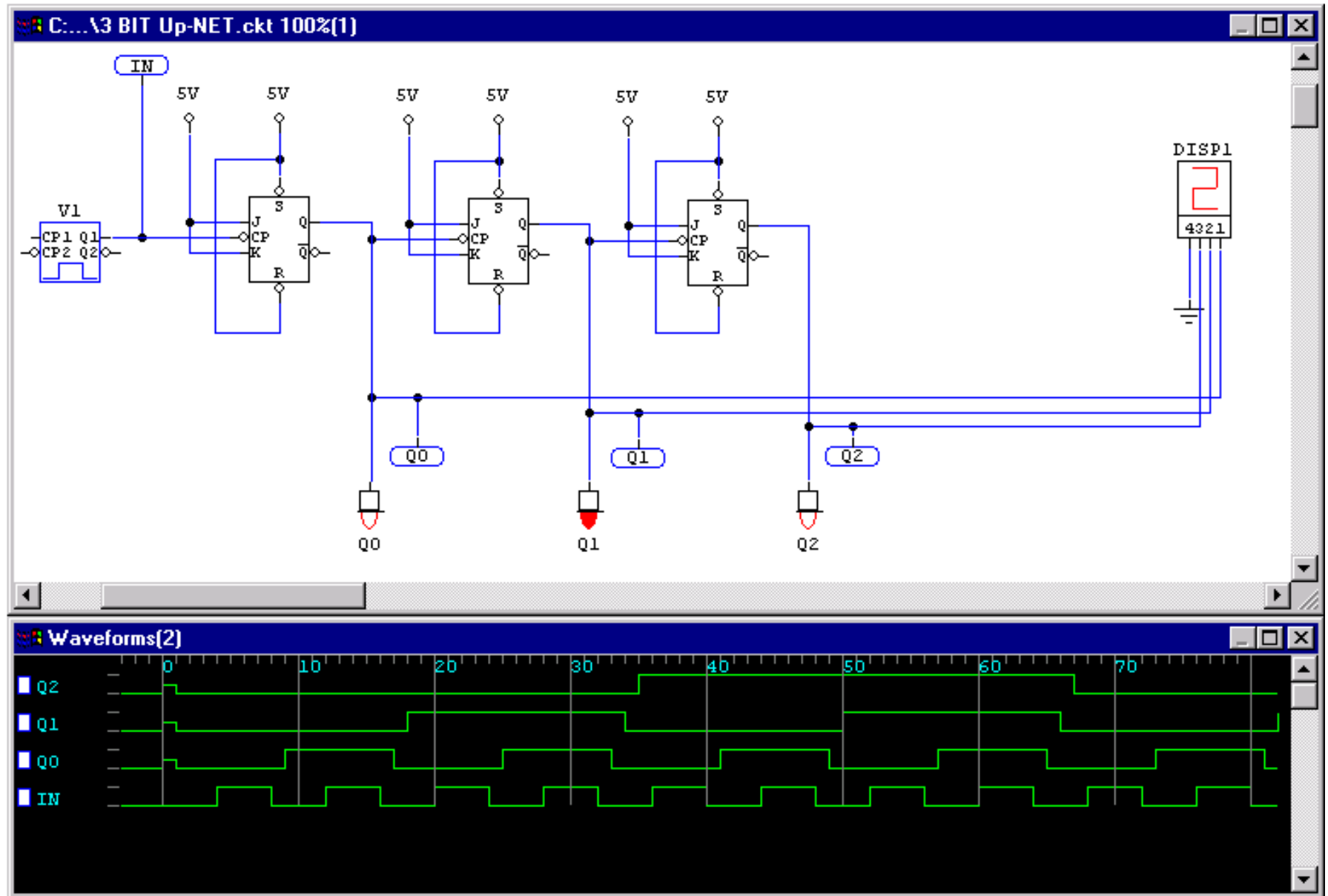

Modulus-6 Counter

