

**AKDENİZ UNIVERSITY**  
**Computer Engineering Department**  
**CSE 211 Digital Design (2024-2025 Fall)**



---

**Lab01 - Digital Logic Gates – 14.10.2024**

---

	Student No	Student Full Name	Group No
1			
2			
3			
4			

### Lab Study 1

In this experiment, you will work with logic gates from the following integrated circuits: 7404 (NOT), 7400 (NAND), 7408 (AND), 7432 (OR), and 7486 (XOR). The pins labeled A and B will serve as inputs, while the pin labeled Q will be the output.

Using the switches corresponding to A and B, you will apply logic levels (0 and 1) to the gate inputs and observe the output behavior. Additionally, you will incorporate the 7404 (NOT) gate, where pin A will be used as the input and pin Q as the output. Apply the specified input conditions to these gates and carefully record the resulting outputs in Table 1.

Ensure to fill in Table 1 with the correct truth tables for each of the logic gates tested.


Table 1 - Truth Table of Logic Gates

A	B	Q1 (NOT)	Q2 (NAND)	Q3 (AND)	Q4 (OR)	Q5 (XOR)
0	0					
0	1					
1	0					
1	1					

## LOGIC GATE PINOUTS


### NOT Gate

#### 74LS04 Pinout

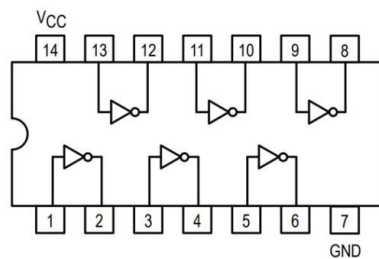


### NAND Gate

#### 74LS00 Pinout

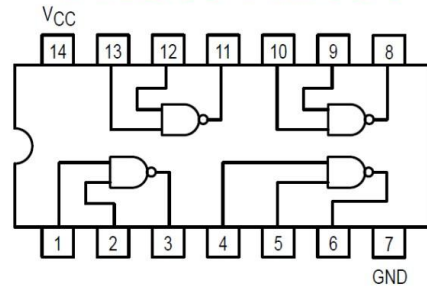


### AND Gate

#### 74LS08 Pinout

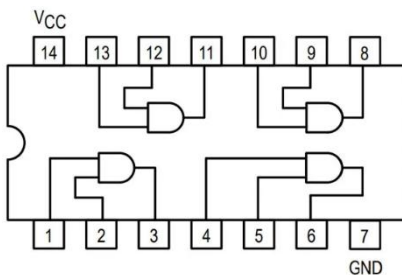


### OR Gate

#### 74LS32 Pinout

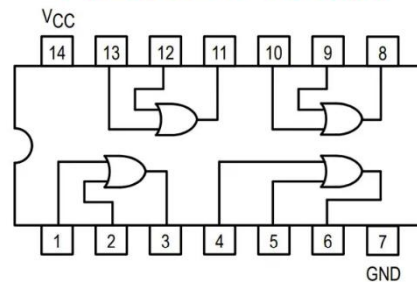

### NOR Gate

#### 74LS02 Pinout

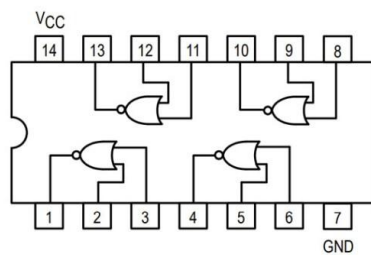

### XOR Gate

#### 74LS86 Pinout

