

# CSE211 Digital Design

Akdeniz University

Week11: Combinational Logic Part 2

Assoc.Prof.Dr. Taner Danişman

tdanisman@akdeniz.edu.tr


# Course program

2

Week 01	2-Oct-23	Introduction
Week 02	9-Oct-23	Digital Systems and Binary Numbers I
Week 03	16-Oct-23	Digital Systems and Binary Numbers II
Week 04	23-Oct-23	Boolean Algebra and Logic Gates I
Week 05	30-Oct-23	Boolean Algebra and Logic Gates II
Week 06	6-Nov-23	Gate Level Minimization
Week 07	13-Nov-23	Karnaugh Maps
Week 08	20-Nov-23	Midterm
Week 09	27-Nov-23	Karnaugh Maps
Week 10	4-Dec-23	Combinational Logic
Week 11	11-Dec-23	Combinational Logic
Week 12	18-Dec-23	Timing, delays and hazards
Week 13	25-Dec-23	Synchronous Sequential Logic
Week 14	1-Jan-24	Synchronous Sequential Logic

# Binary Multiplier

3

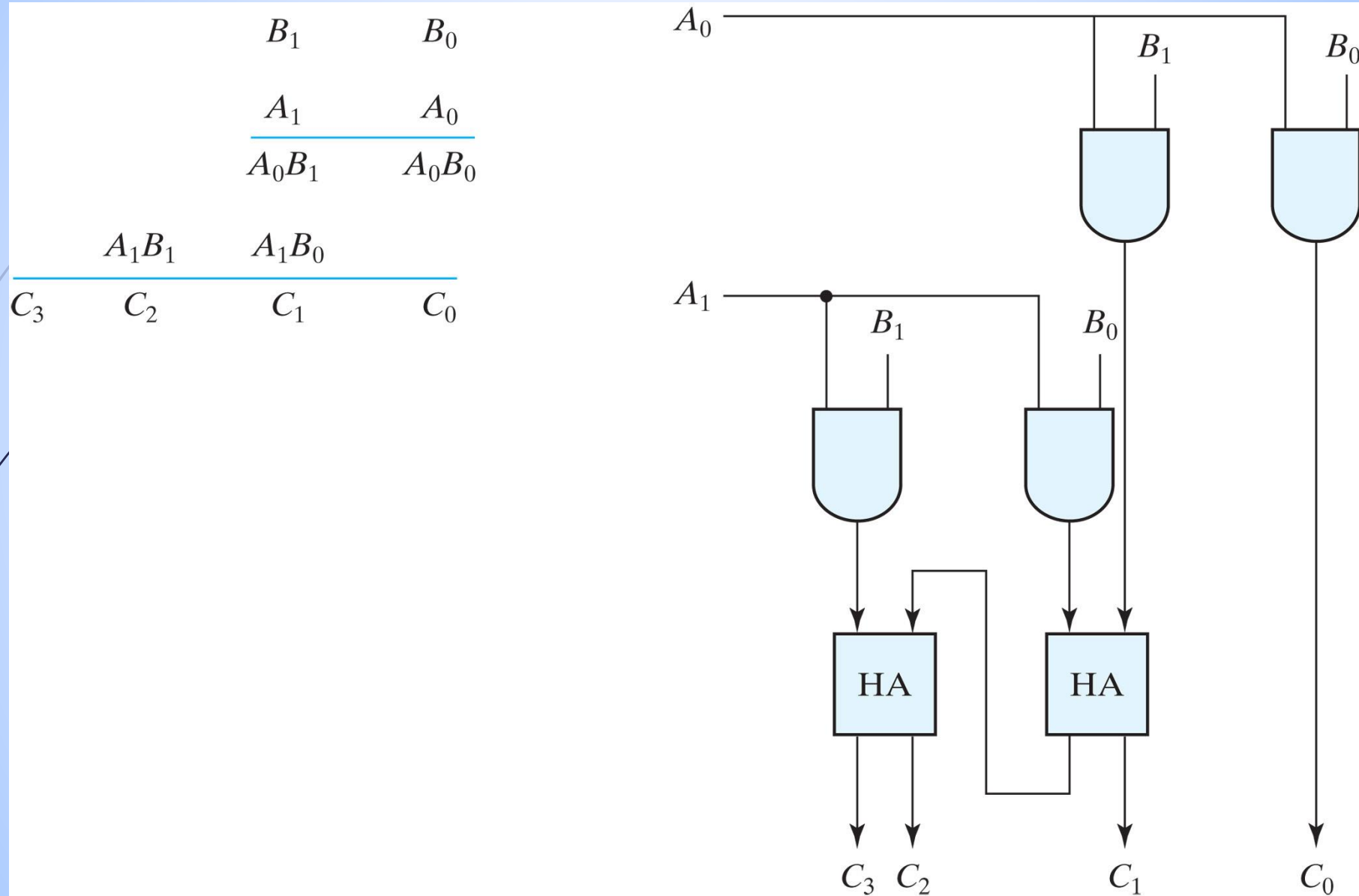

# Binary Multiplier

4


- For  **$J$**  multiplier bits and  **$K$**  multiplicand bits, we need
  - $(J \times K)$  AND gates and
  - $(J - 1)$   **$K$ -bit adders** to produce a product of  $(J + K)$  bits.

MULTPLICAND	→	6
MULTIPLIER	×	3
<hr/>		
PRODUCT	→	18

5
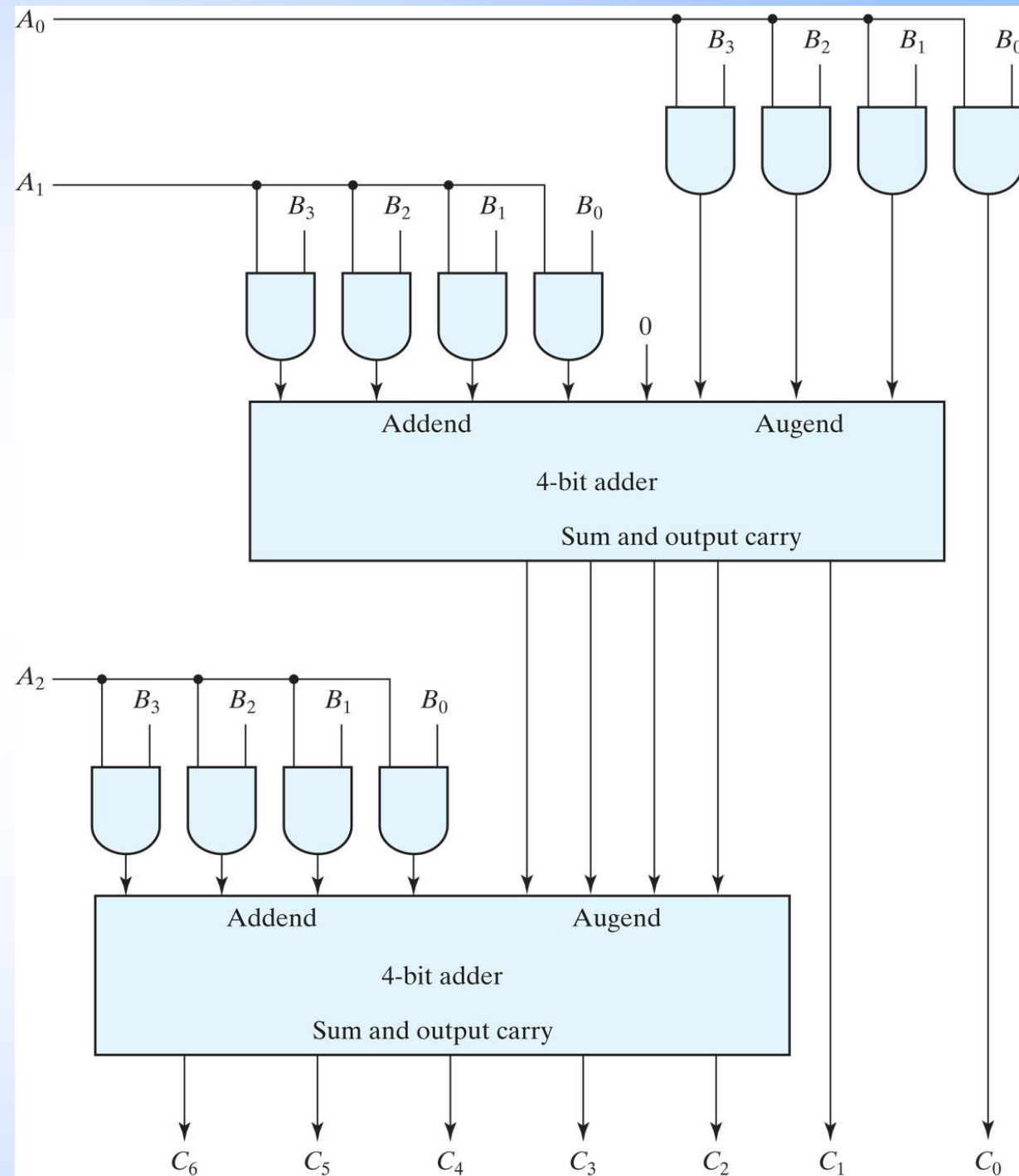
# Four-bit by Three bit multiplier

- $B_3B_2B_1B_0$  by  $A_2A_1A_0$
- Since  $K = 4$  and  $J = 3$ , we need **12 AND gates** and **two 4-bit adders** to produce a product of **seven bits**



# Magnitude Comparator

6


- The comparison of two numbers is an operation that determines whether one number is greater than, less than, or equal to the other number.
- **Magnitude comparator** is a combinational circuit that compares two numbers  $A$  and  $B$  and determines their relative magnitudes.
  - $A > B$
  - $A = B$
  - $A < B$

# Magnitude Comparator

7

A	B	A>B	A=B	A<B
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

What about more than one bit?

 



# Magnitude Comparator

8

- The circuit for comparing two  $n$ -bit numbers has  **$2^{2n}$  entries** in the truth table and becomes too cumbersome, even with  $n = 3$ .
- $A=B$  ( X-NOR Solution)

$$x_i = A_i B_i + A'_i B'_i \quad \text{for } i = 0, 1, 2, 3$$

$$(A = B) = x_3 x_2 x_1 x_0$$

- To determine whether  $A$  is greater or less than  $B$ , we inspect the relative magnitudes of pairs of significant digits, starting from the most significant position.



# Magnitude Comparator

9


- Greater than and less than

$$(A > B) = A_3B'_3 + x_3A_2B'_2 + x_3x_2A_1B'_1 + x_3x_2x_1A_0B'_0$$

$$(A < B) = A'_3B_3 + x_3A'_2B_2 + x_3x_2A'_1B_1 + x_3x_2x_1A'_0B_0$$

- The symbols  $A > B$  and  $A < B$  are *binary* output variables that are equal to 1 when  $A > B$  and  $A < B$ , respectively.

# 4-bit Magnitude Comparator

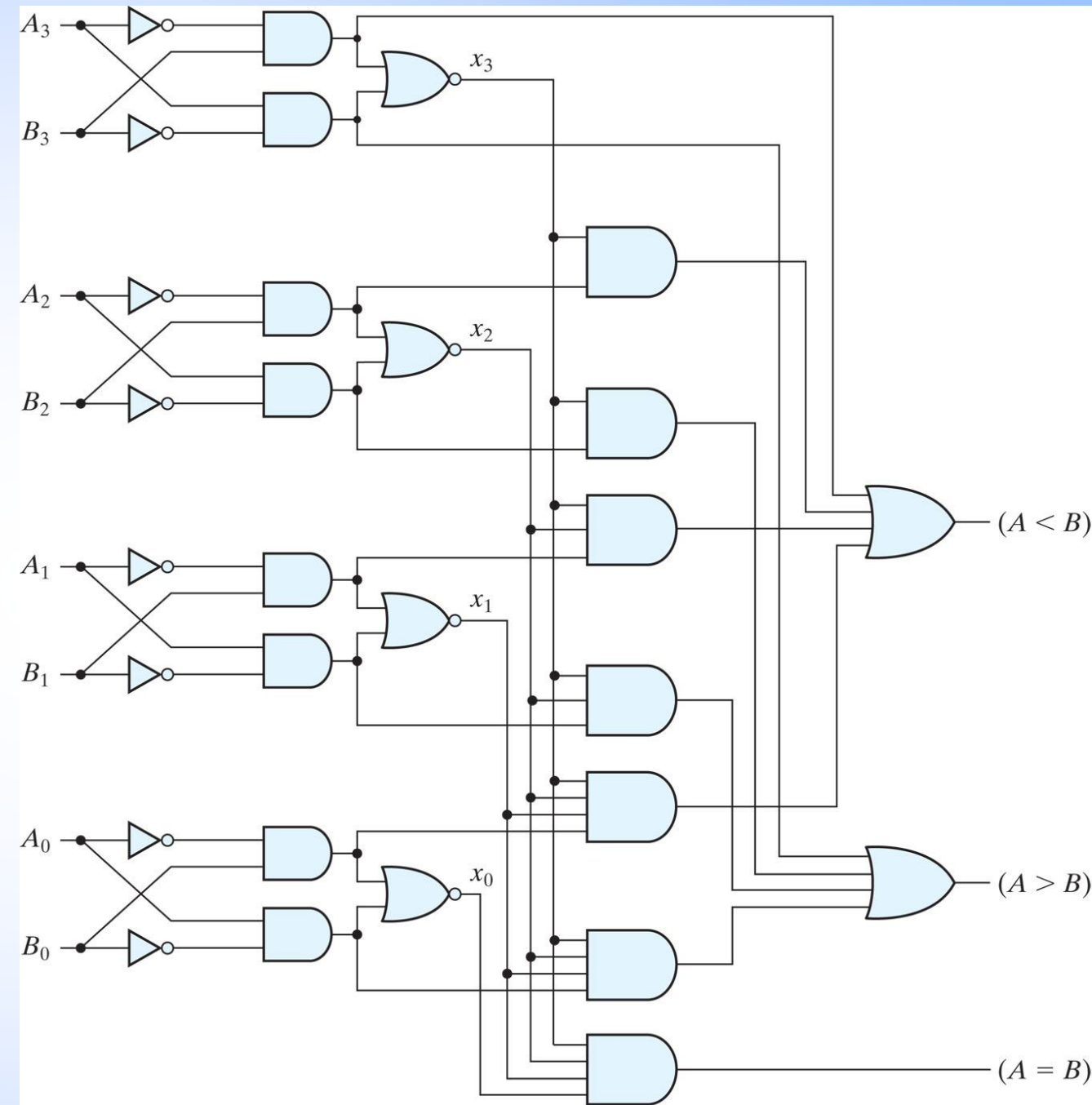

# Decoders


11

- ▶ A binary code of  $n$  bits is capable of representing up to  $2^n$  **distinct elements** of coded information.
- ▶ A **decoder** is a **combinational circuit** that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines.
- ▶ If the  $n$ -bit coded information has **unused** combinations, the decoder may have fewer than  $2^n$  outputs.
- ▶ Their purpose is to generate the  $2^n$  (or fewer) **minterms** of  $n$  input variables
- ▶ The name **decoder** is also used in conjunction with other code converters, such as a **BCD-to-seven-segment decoder**
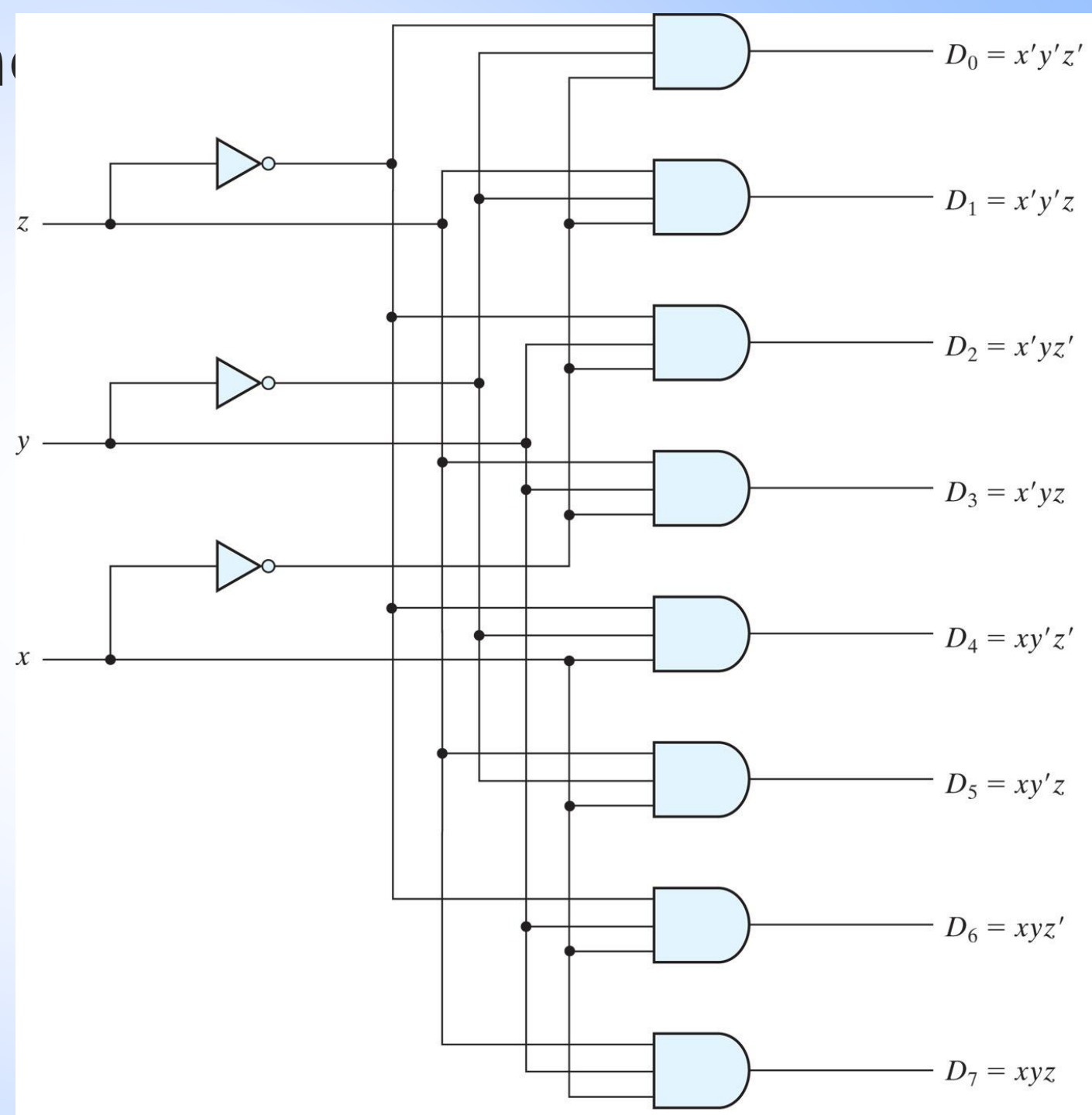
# Three-to-eight-line

12

- ▶ A particular application of this decoder is binary-to-octal conversion



# Three-to-eight-line decoder

13


**Table 4.6**

*Truth Table of a Three-to-Eight-Line Decoder*

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>	<i>D</i> <sub>4</sub>	<i>D</i> <sub>5</sub>	<i>D</i> <sub>6</sub>	<i>D</i> <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

# Two-to-four-line Decoders with Enable

14

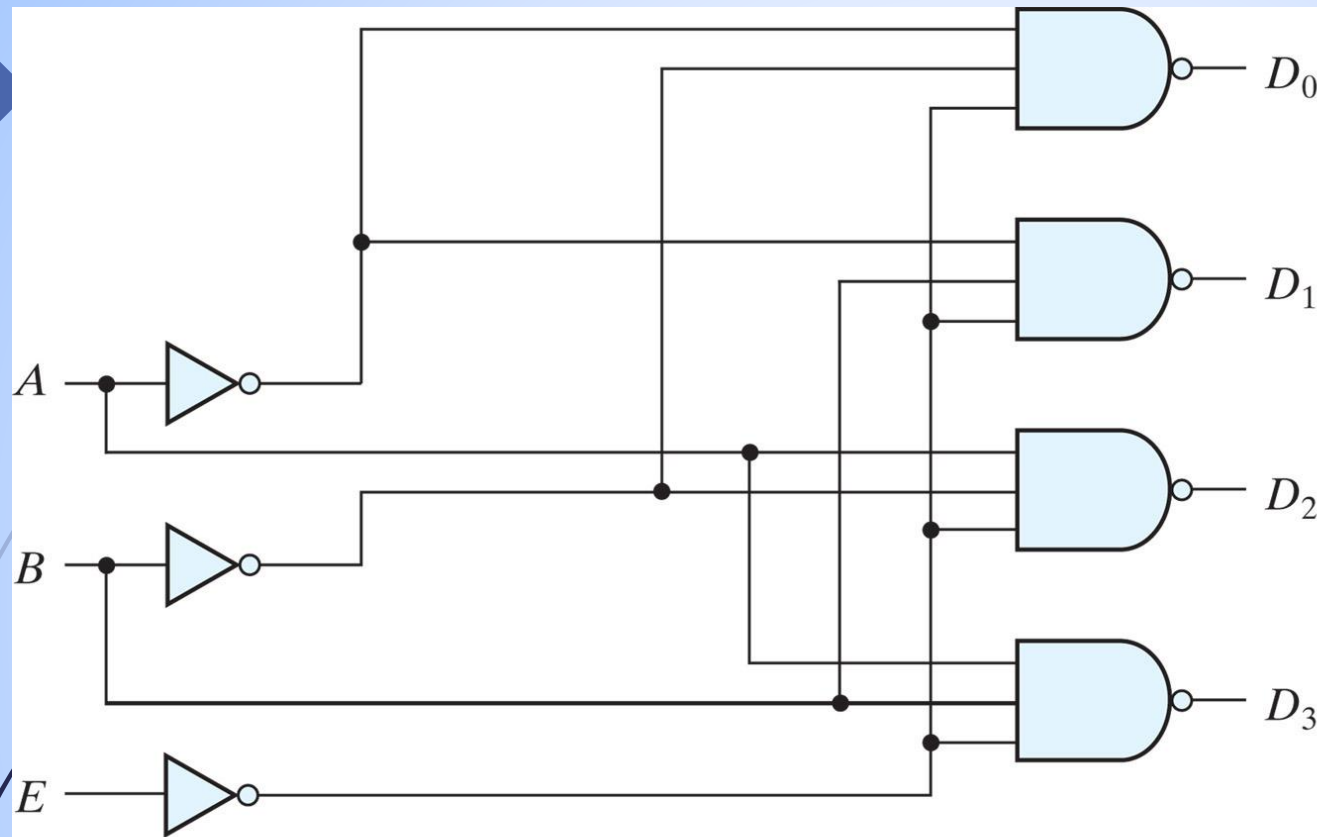

(a) Logic diagram

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table


Copyright ©2013 Pearson Education, publishing as Prentice Hall

- A decoder **with enable input** can function as a **demultiplexer**
- **Demultiplexer**: A circuit that receives information from a **single line** and directs it to one of **2<sup>n</sup>** possible output lines.


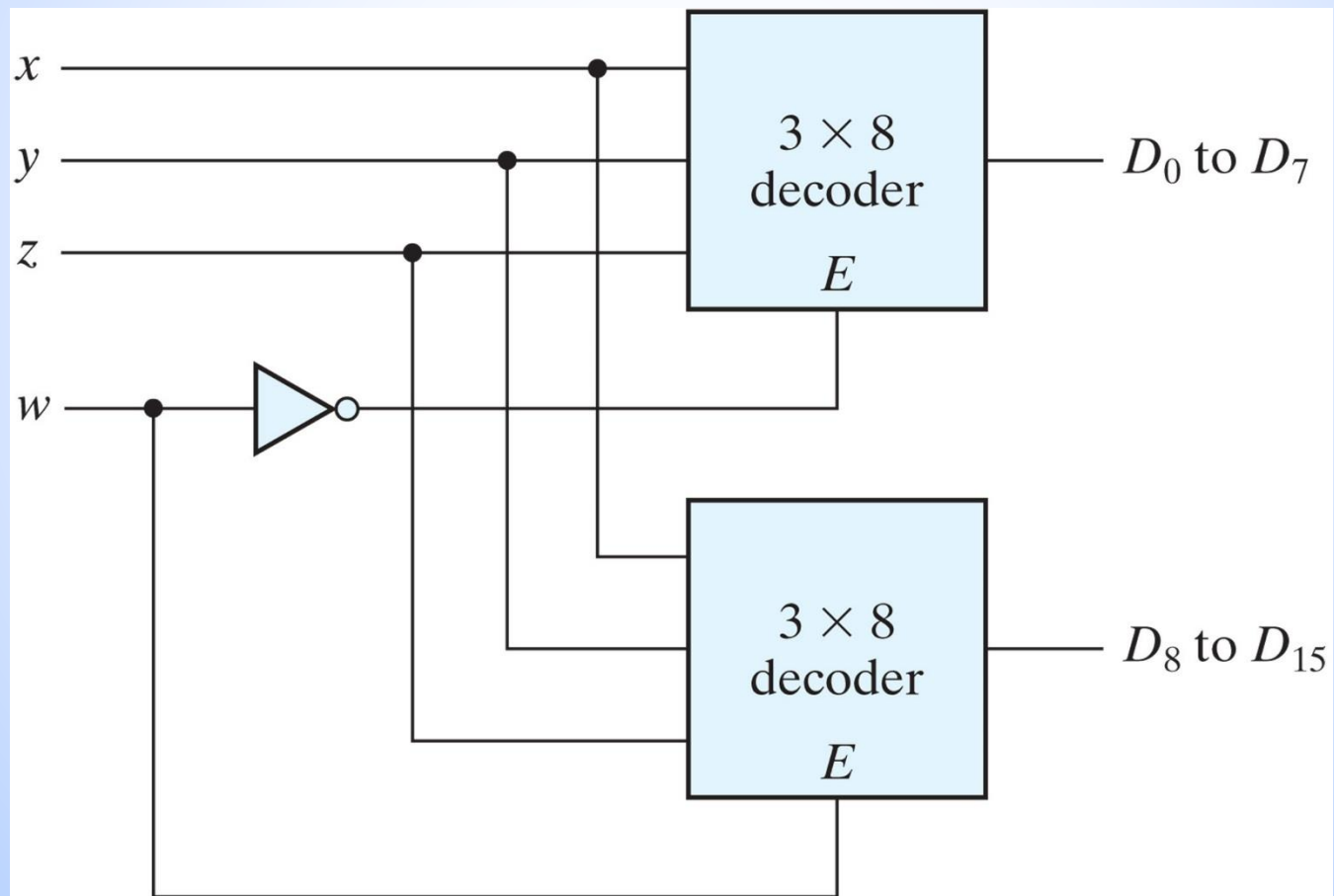
# 4 × 16 decoder constructed with two 3 × 8 decoders

- Decoders with enable inputs can be connected together to form a larger decoder circuit.





# Combinational Logic Implementation

16

- Since any Boolean function can be expressed in sum-of-minterms form, a decoder that generates the minterms of the function, together with an external OR gate that forms their logical sum, provides a hardware implementation of the function.

**Table 4.4**  
*Full Adder*

<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$


# Implementation of a full adder with a decoder

17

- The OR gate for output  $S$  forms the logical sum of minterms 1, 2, 4, and 7.
- The OR gate for output  $C$  forms the logical sum of minterms 3, 5, 6, and 7.

$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$

 

# Implementation of a full adder with a decoder

- ▶ A function with a long list of minterms requires an OR gate with a large number of inputs.
- ▶ A function having a list of  $k$  minterms can be expressed in its complemented form  $F$  with  $2^n - k$  minterms. If the number of minterms in the function is greater than  $2^n/2$  then  $F$  can be expressed with fewer minterms.
- ▶ In such a case, it is advantageous to use a **NOR gate** to sum the minterms of  $F$ .

# 4.10 Encoders

19

- An encoder is a digital circuit that performs the **inverse operation of a decoder**
- An encoder has  $2^n$  (or fewer) input lines and  $n$  output lines
- The output lines, as an aggregate, generate the binary code corresponding to the input value

# Octal-to binary Encoder example

20

- The encoder can be implemented with three OR gates

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

**Table 4.7**  
*Truth Table of an Octal-to-Binary Encoder*

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1



# Octal-to binary Encoder example

21

- The problem:
  - It has the limitation that only one input can be active at any given time
  - If two inputs are active simultaneously, the output produces an undefined combination
- For example, if  $D_3$  and  $D_6$  are 1 simultaneously, the output of the encoder will be 111 because all three outputs are equal to 1
- **The output 111 does not represent either binary 3 or binary 6**
- To resolve this ambiguity, encoder circuits must establish an **input priority** to ensure that **only one input is encoded**
- If both  $D_3$  and  $D_6$  are 1 at the same time, the output will be **110** because  $D_6$  has higher priority than  $D_3$
- **Another ambiguity** in the octal-to-binary encoder is that an output with all 0's is generated when all the inputs are 0; but this output is the same as when  $D_0$  is equal to 1.

# Priority Encoder

22

- If two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence.
- **Valid** bit indicator is set to 1 when one or more inputs are equal to 1. If all inputs are 0, there is no valid input and  $V$  is equal to 0.
- Input  $D_3$  has the highest priority, so, regardless of the values of the other inputs, when this input is 1, the output for  $xy$  is 11 (binary 3)

**Table 4.8**  
*Truth Table of a Priority Encoder*

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1




# Maps for a Priority Encoder

23



**Table 4.8**

*Truth Table of a Priority Encoder*

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

 

$x =$

  

$y =$



# Four-bit Priority Encoder

24

$$x = D_2 + D_3$$

$$y = D_3 + D_1 D_2'$$


$$V = D_0 + D_1 + D_2 + D_3$$

**Table 4.8**

*Truth Table of a Priority Encoder*

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

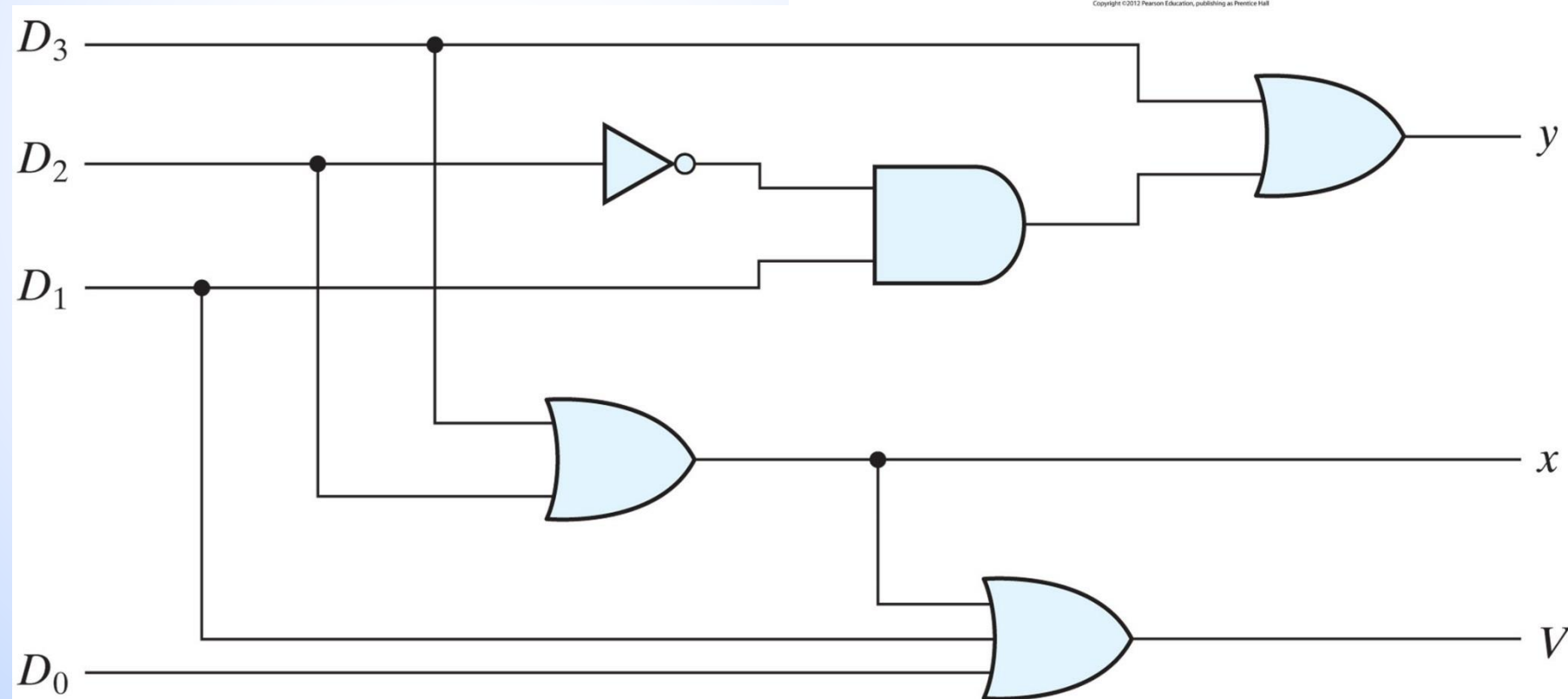Copyright ©2012 Pearson Education, publishing as Prentice Hall



Copyright ©2013 Pearson Education, publishing as Prentice Hall

# 4.11 Multiplexers


25

- A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line.
- There are  $2^n$  input lines and  $n$  selection lines whose bit combinations determine which input is selected
- **The multiplexer acts like an electronic switch that selects one of the sources**
- The multiplexer is often labeled “**MUX**” in block diagrams
- A multiplexer is also called a **data selector**

 
# Two-to-one line multiplexer

26

- ▶ A two-to-one-line multiplexer connects one of two 1-bit sources to a common destination




(a) Logic diagram

 

(b) Block diagram

# Four-to-one line multiplexer

27

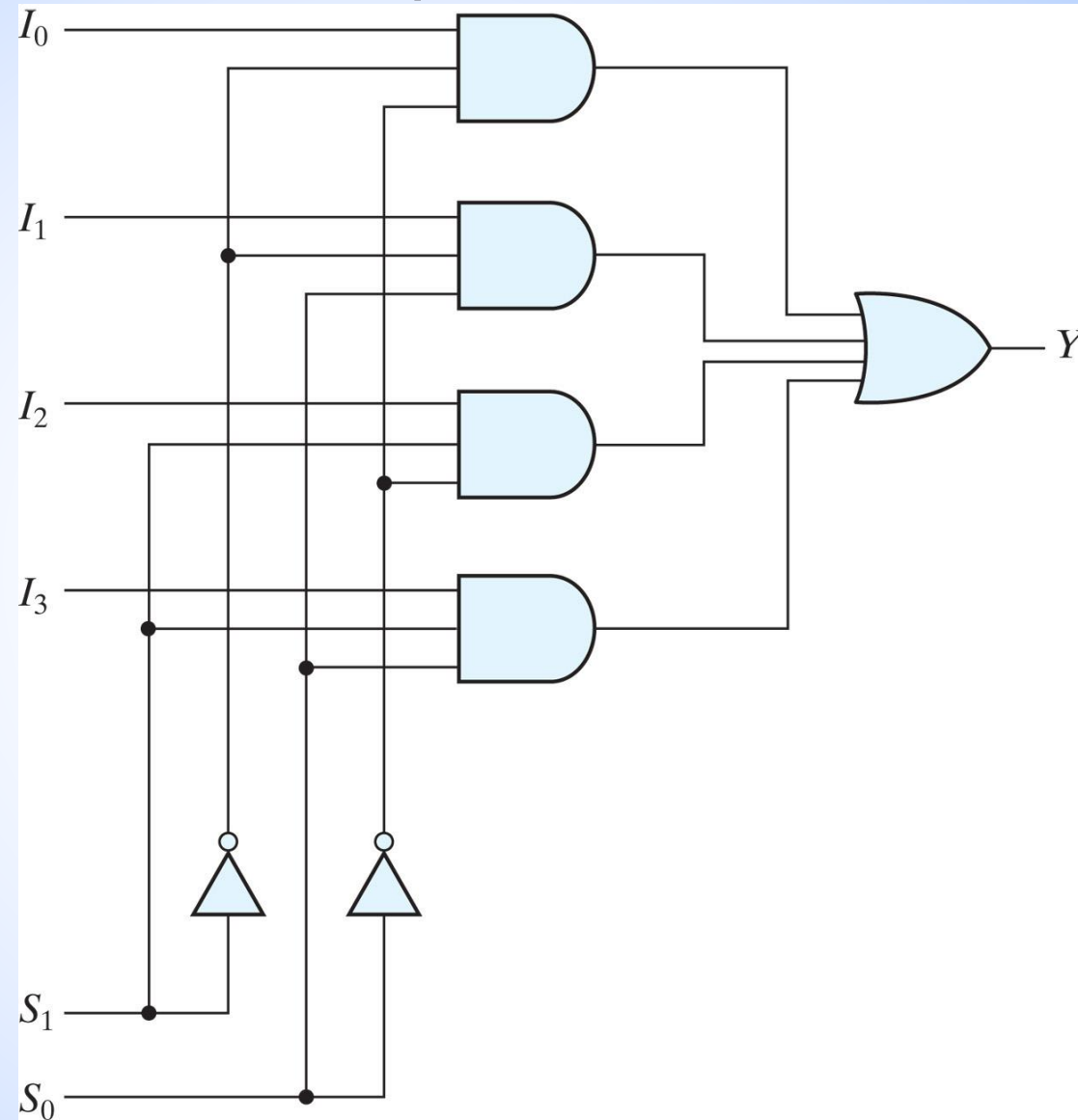

(a) Logic diagram

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$


(b) Function table

# Implementing a Boolean function with a multiplexer

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$

$x$	$y$	$z$	$F$	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table


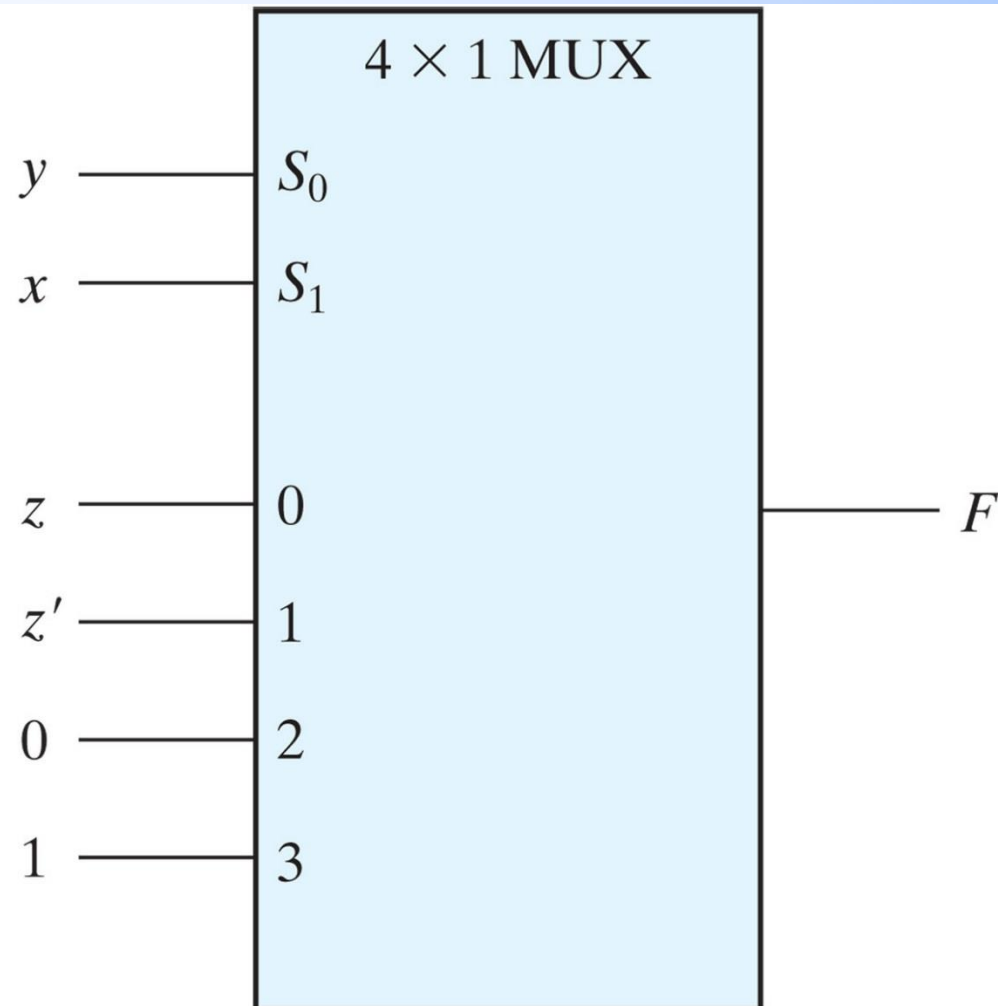


(b) Multiplexer implementation
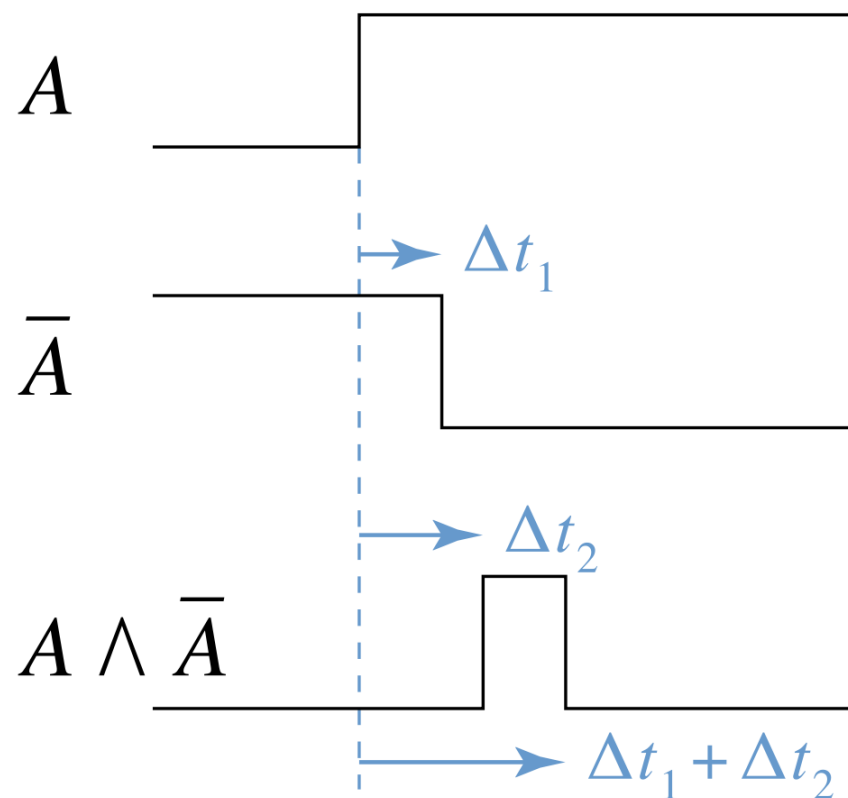 
# Hazards

When the input to a combinational logic circuit changes, unwanted switching transients may appear on the output.

These transients occur when different paths from input to output have different propagation delays.





# Hazards

- When analyzing combinational logic circuits for hazards we will consider the case where only one input changes at a time.
- Under this condition, a static 1-hazard occurs when the input change causes one product term (in a SOP expression) to transition from 1 to 0 and another product term to transition from 0 to 1.
- Both product terms can be transiently 0, resulting in the static 1-hazard.


# Timing hazard

31

- There is a delay for the logic gates
- When they dd up together they create timing hazards.
  - $t_{pLH}$  = low-to-high,  $t_{pHL}$  = high-to-low
- **Three types exist**
  - **Static-0:** Wxpected 0 but received 1 for a short period of time. It occurs in POS circuits
  - **Static 1:** Expected 1 received 0 for a short period of time. It occurs on POS circuits.
  - **Dynamic:** Multiple changses in the output before stable.



Statik 0

 

Statik 1



Dinamik


# Sample question

32

(inverter) **5ns**, AND gate **10ns**.

Initially  $X=0$ .  $X$  became 1 for 80ns then become 0

 
Draw a timing diagram showing changes in  $X$ ,  $Y$  ve  $Z$


 
# Solution

33



- ▶ Draw an empty timing diagram
- ▶ Show the formula for the circuit
  - ▶  $Z = XY = XZ'$
- ▶ Show initial values of X and Y
- ▶ Draw the rest considering the gate delays




(inverter) **5ns**, AND gate **10ns** delay.

Initially **X=0 Y=1**

  What if for **80ns X=1** and then becomes 0



# Hazards

 

# Hazards

- Under the same condition, a static 0-hazard occurs when the input change causes one sum term (in a POS expression) to transition from 0 to 1 and another sum term to transition from 1 to 0.
- Both sum terms can be transiently 1, resulting in the static 0-hazard.




# Detecting Static 1-Hazards

We can detect hazards in a two-level AND-OR circuit using the following procedure:


1. Write down the sum-of-products expression for the circuit.
2. Plot each term on the map and loop it.
3. If any two adjacent 1's are not covered by the same loop, a 1-hazard exists for the transition between the two 1's. For an  $n$ -variable map, this transition occurs when one variable changes and the other  $n - 1$  variables are held constant.



# Detecting Static 1-Hazards

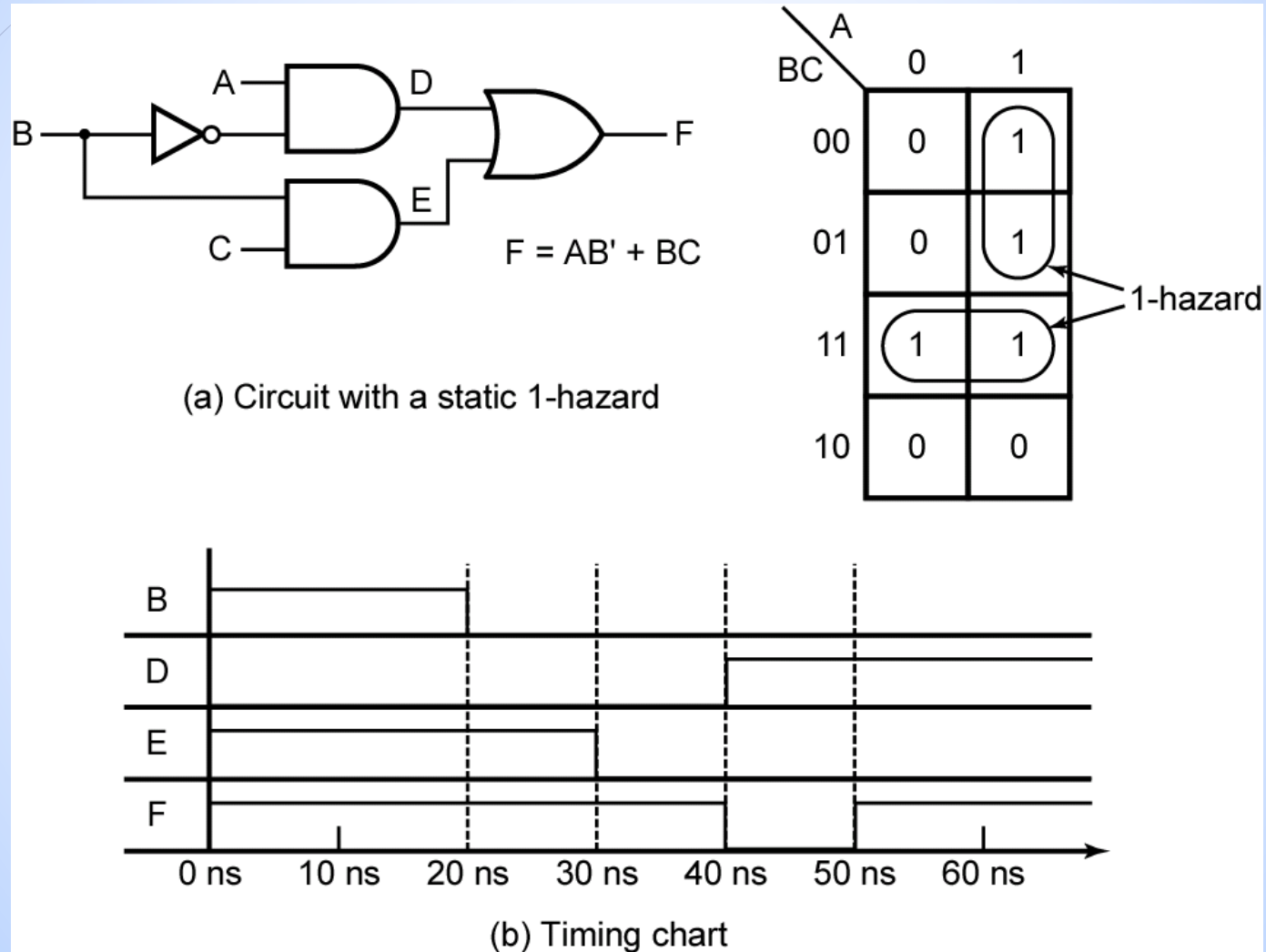

# Removing Static 1-Hazards

 


# Detecting Static 0-Hazards

We can detect hazards in a two-level OR-AND circuit using the following procedure:

1. Write down the product-of-sums expression for the circuit.
2. Plot each sum term on the map and loop the zeros.
3. If any two adjacent 0's are not covered by the same loop, a 0-hazard exists for the transition between the two 0's. For an  $n$ -variable map, this transition occurs when one variable changes and the other  $n - 1$  variables are held constant.

# Detecting Static 0-Hazards

 

# Removing Static 0-Hazards

41

