

CSE211 Digital Design

Akdeniz University

Week13: Sequential Logic Part 2

1

Assoc.Prof.Dr. Taner Danişman

tdanisman@akdeniz.edu.tr


5.4 Storage Elements: Flip-Flops

2

- The state of a latch or flip-flop is switched by a change in the control input. This momentary change is called a **trigger**
- The problem with the latch is that it responds to a change in the *level* of a clock pulse. Glitches are problematic.

Clock response in latch and flip-flop

3

 

(a) Response to positive level



(b) Positive-edge response




(c) Negative-edge response

Flip-Flops


- The latch timing problem
- Edge-triggered flip-flop
- Master-slave flip-flop
- Direct inputs to flip-flops
- Flip-flop timing

The Latch Timing Problem

➤ Consider the following circuit:

 

➤ Suppose that initially $Y = 0$.

 

- As long as $C = 1$, the value of Y continues to change!
- The changes are based on the delay present on the loop through the connection from Y back to Y .
- This behavior is clearly unacceptable.
- Desired behavior: Y changes only once per clock pulse

Master-slave D flip-flop

6

- The circuit samples the D input and **changes** its output Q only at the **negative edge** of the synchronizing or controlling clock.
- Another say, a change in the output of the flip-flop can be triggered only by and during the transition of the clock from 1 to 0.

